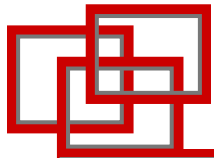


LISTEN.
THINK.
SOLVE.SM

Harmonic Mitigation for Variable Frequency Drives


HWEA Conference
February 15, 2011

Kelvin J. Hurdle
Rockwell Bus. Dev. Mgr.





OVERVIEW

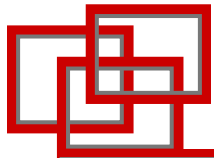- Linear vs. Non- Linear Load Definitions
- AC Drive Input Current Harmonics
- Potential Affects of Harmonics
- Application of Harmonic Industry Standards, IEEE Std. 519-1992
- Harmonic Mitigation Techniques




Drive System

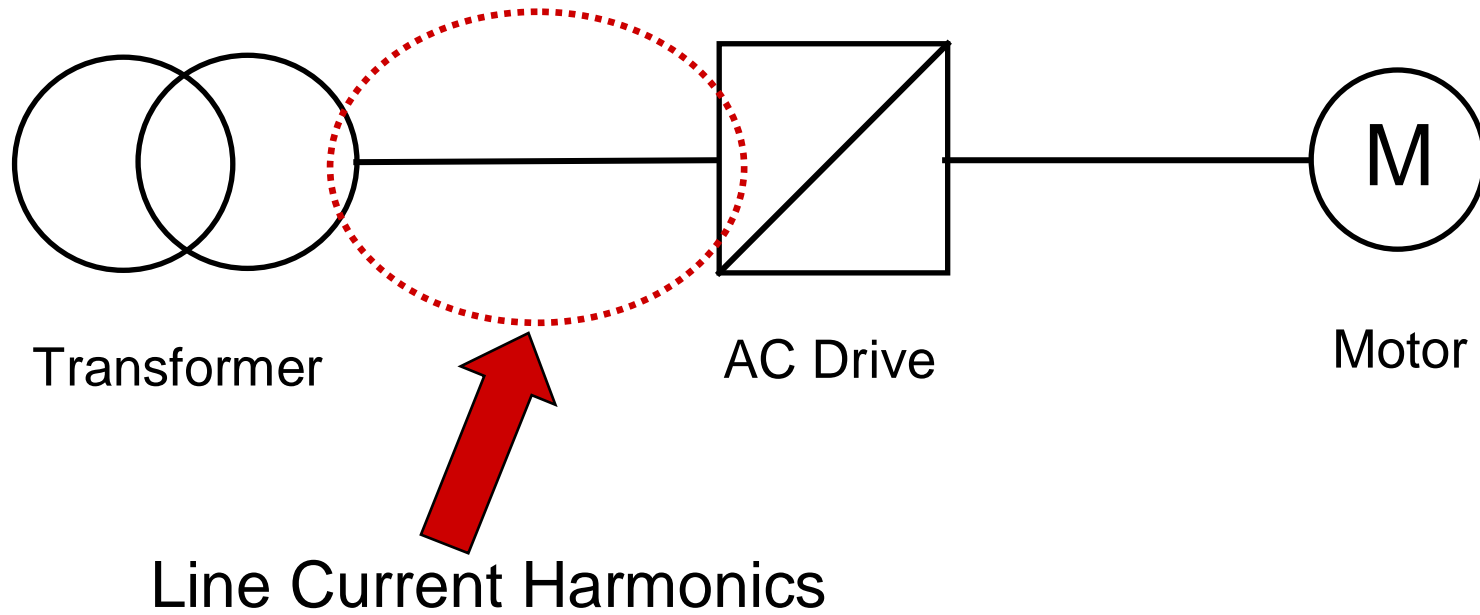


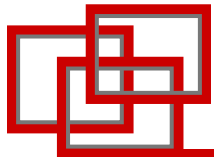


PWM AC Drive with 6-Pulse Rectifier

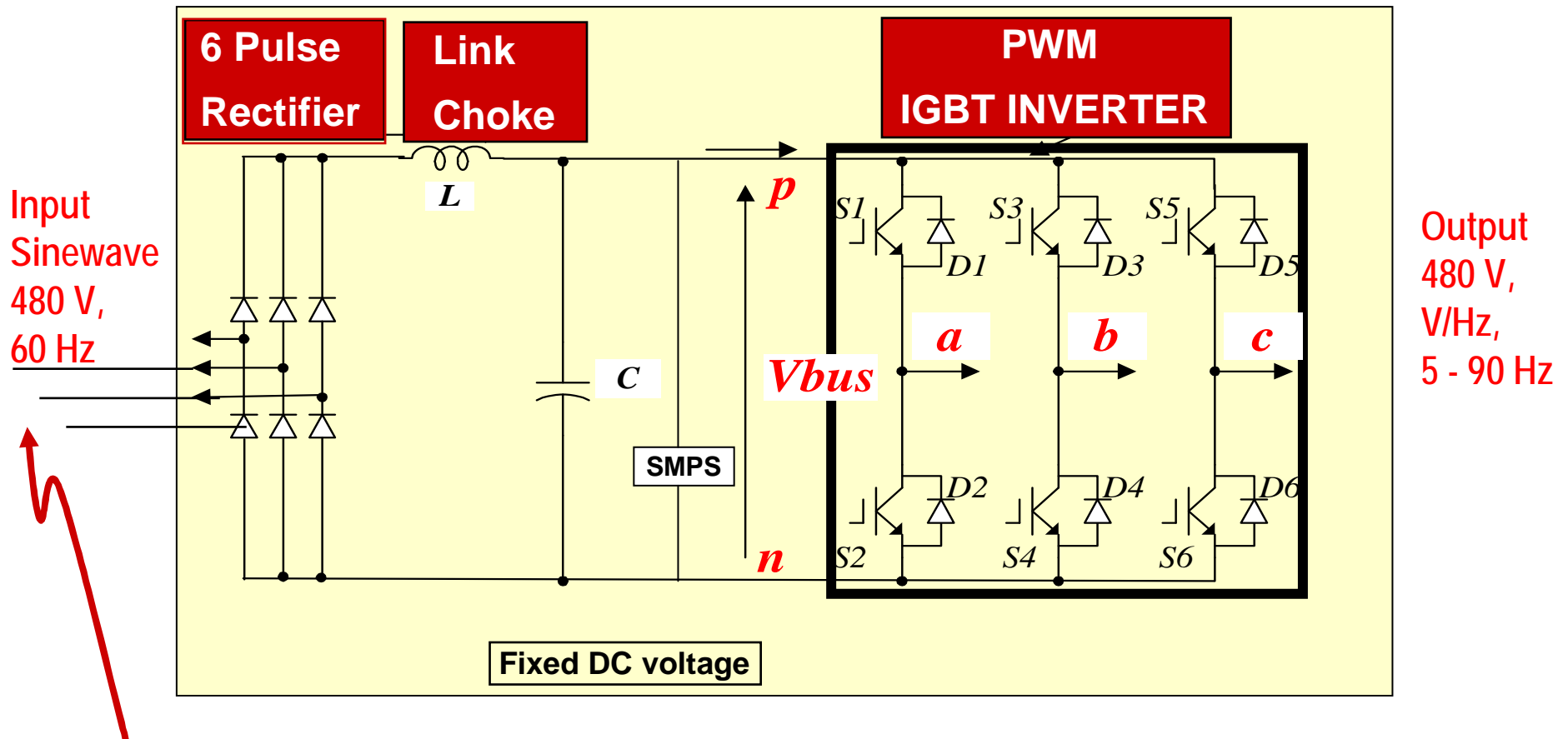


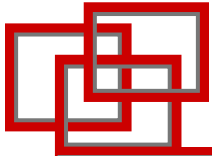Utility Input current to a 6-pulse rectifier is non-sinusoidal and produces current harmonics which flow back into the power system



What are Harmonics?

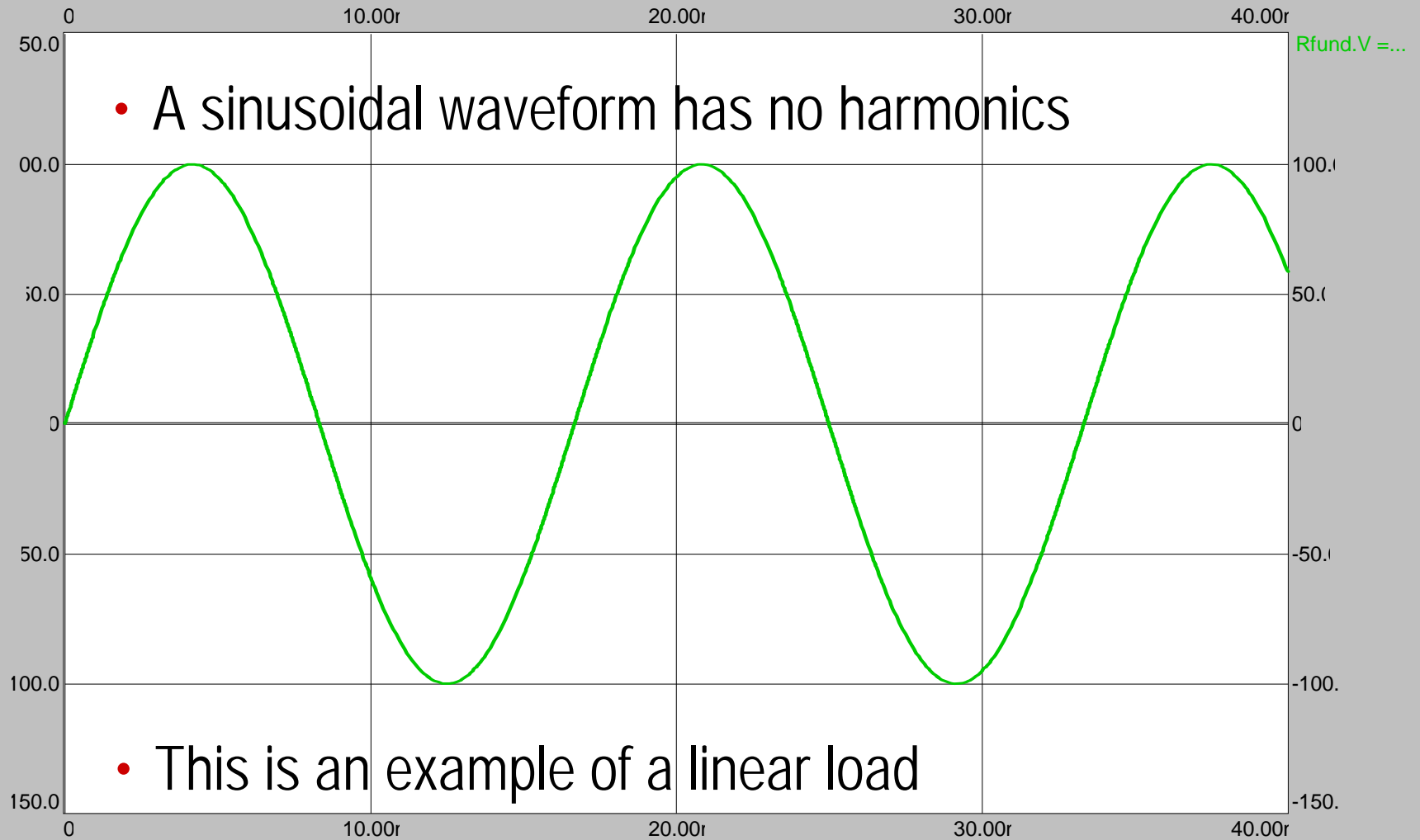

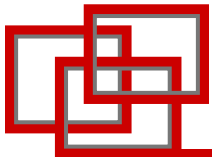

What is a Linear Load?

Linear Load:

Current waveshape linearly follows the Utility sinewave


Voltage waveform

Current can differ in magnitude & power factor phase angle


Linear Commercial Loads:


- Induction motors
- Incandescent lights
- Resistance heaters
- Electromagnetic devices
- Transformers (non-linear with over-voltage)

Time Domain Analysis

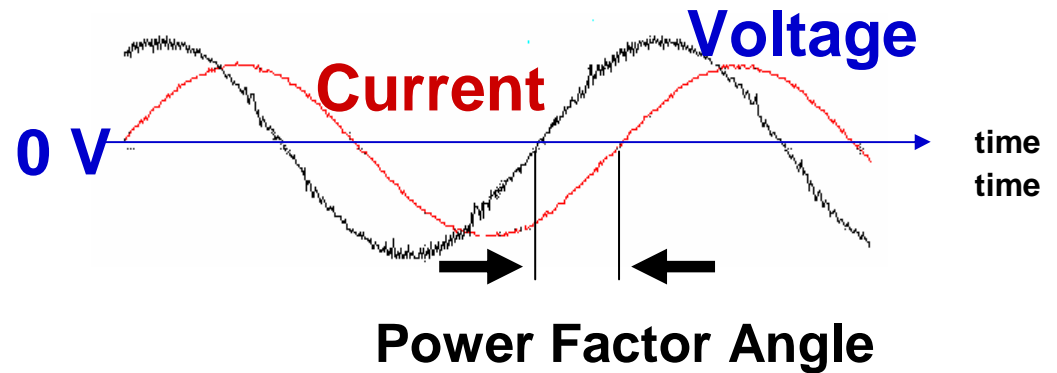



Frequency Domain Analysis

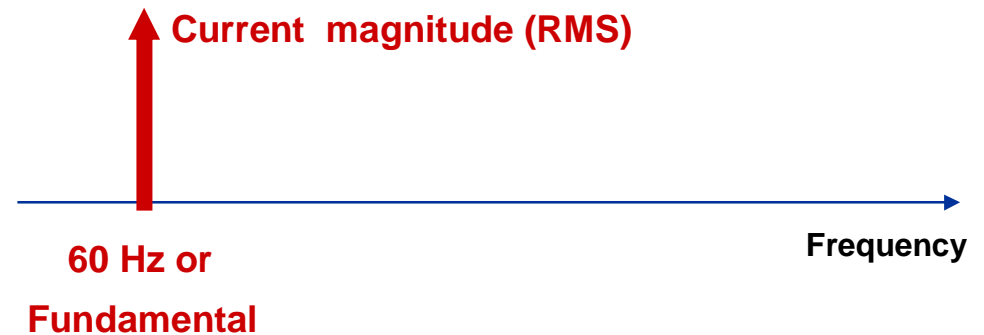

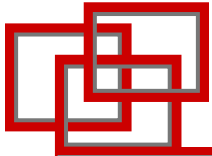

What are Harmonics?

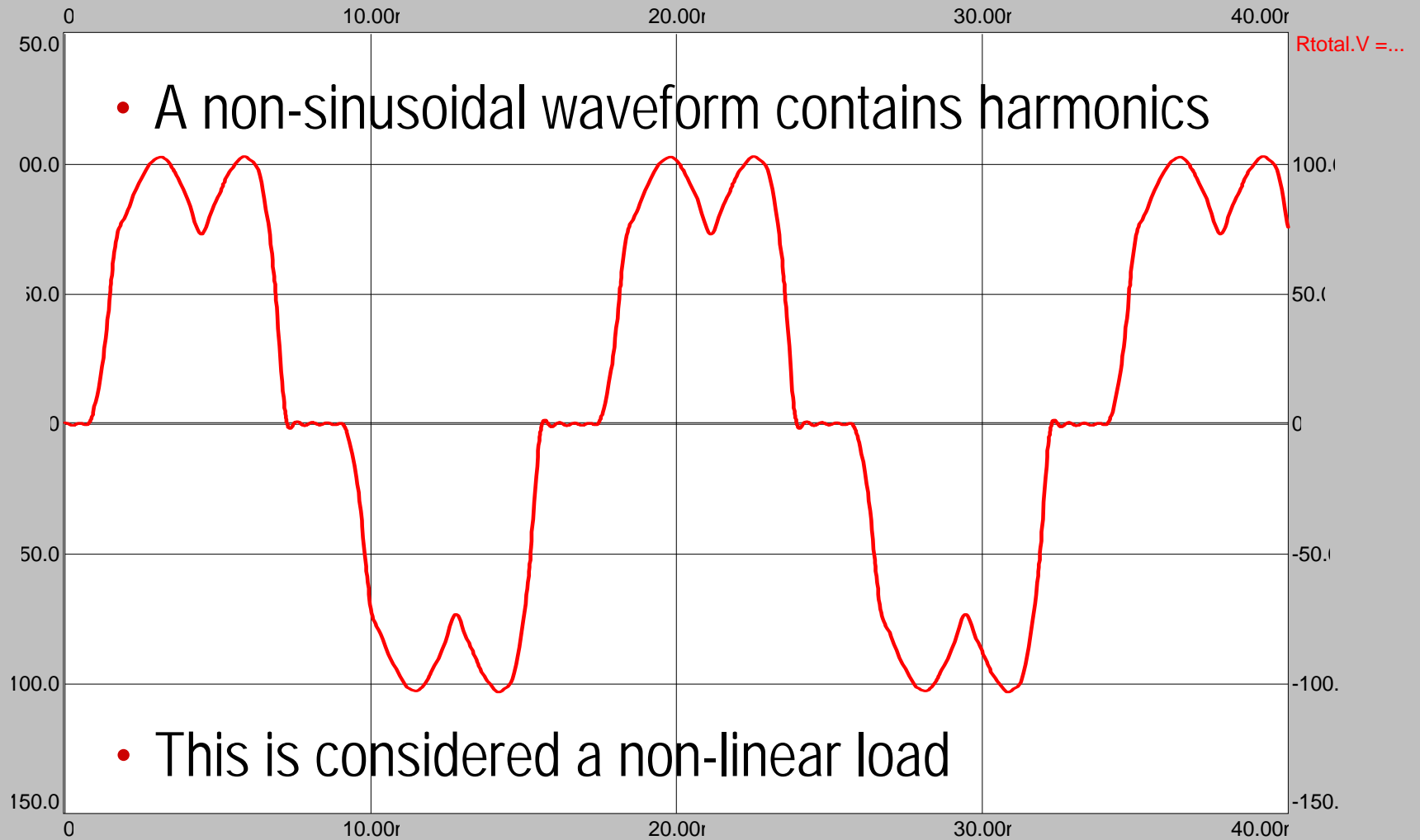

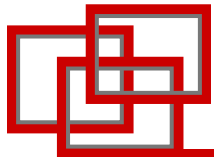

What is a Non-Linear Load?


Harmonics are

Deviations from the Ideal
Fundamental AC line voltage
and current waveforms


Non-linear loads contain


Current Harmonics which
cause *Voltage Harmonic*
problems for other users

Time Domain Analysis

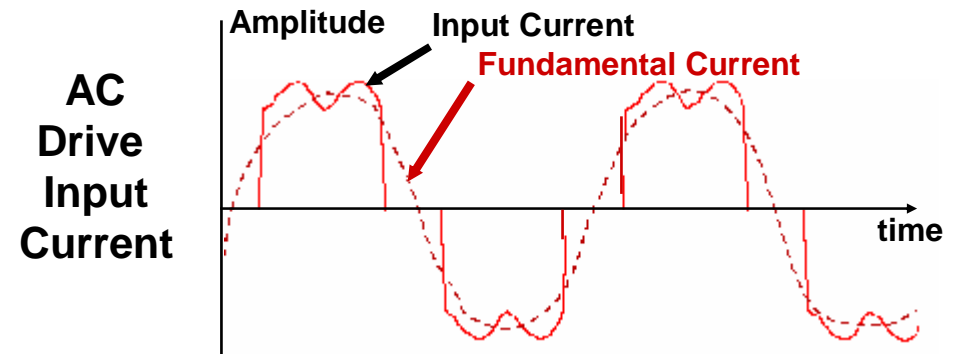

Frequency Domain Analysis

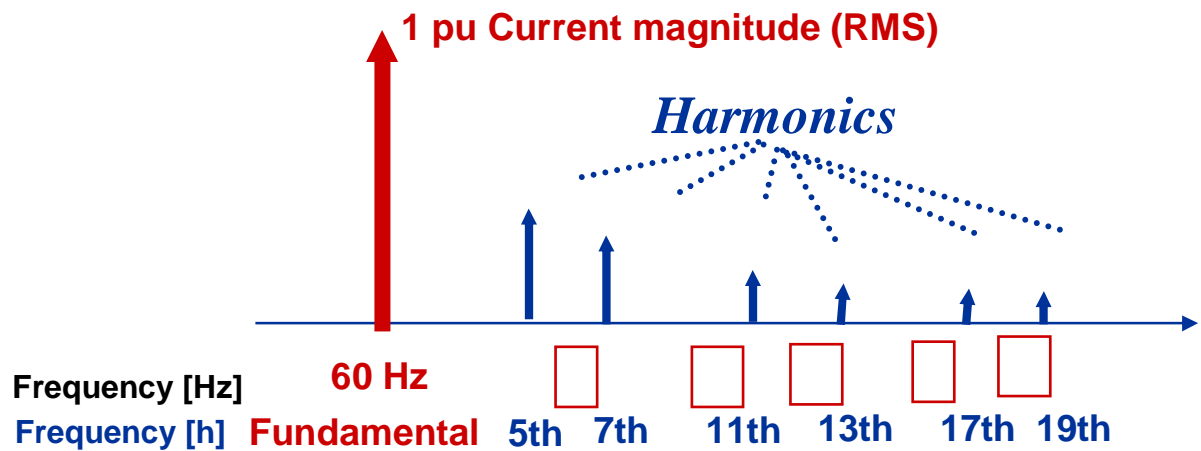

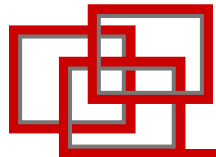


Root Cause of Problems with Other Equipment

Current Harmonics

create

Voltage Distortion

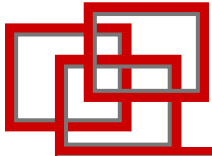

Power Consumer Issues Associated with non-Linear Loads


Non-linear Commercial loads
generally come from:

- Fluorescent lights
- Computers and CRT's
- Fax machines
- And other single phase office equipment

Non-linear Industrial loads
generally come from:


- Welders
- Arc furnaces
- UPS and DC power supplies
- DC Drives & **AC Drives**

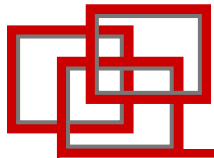- * Fastest growing factory related non-linear load issue is with AC drives
- * This is due to the ever increasing number of installations




What problems do they cause?

- Increased Utility current requirement inability to expand or utilize equipment
- Component overheating distribution transformers & wires
- Nuisance tripping causing lost productivity sensitive equipment
- Equipment malfunction due to multiple or loss of zero crossing
- Noise transfer to other loads possibly even other utility customers
- Incorrect meter readings, relays malfunction maintenance time
- Communication or Telephone Interference problems
- Excitation of Power System Resonance's creating over-voltage's
- Voltage Flat Topping Problem

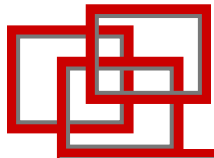

Effects of Harmonics on Power System?

- How are harmonics and power factor related?
 - Harmonics increase the required current supplied
 - Results in increased power requirement from the utility
 - If the total load uses all the utility supplied power, the distribution system is called unity, or 1.0 power factor.
 - If the same load requires more utility supplied power due to harmonics or other losses, then the **power factor decreases**.
 - Some power utilities may impose penalties to the user if they oversize their distribution system due to a poor power factor.

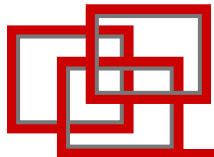


Effect of Harmonics on the Power System?

- How do I determine when I will have a Harmonics Issue with my new or existing Drive Installation ?
- Drives are part of the Non-Linear Load
- If the Non-Linear Load is SIGNIFICANTLY higher than the Linear Load, there is a potential for Harmonic Distortion problems


But how do
I know
what is *SIGNIFICANT*?



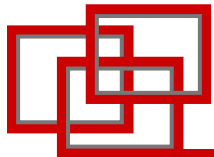

Effect of Harmonics on the Power System?

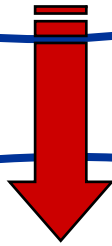Harmonic Currents flowing through the system





Produce Voltage Distortion at various Points of Common Coupling (PCC) with other loads

Voltage Distortion depends upon:


- System Impedance's (% Z)
- Amplitude of the Injected Harmonics


PLANT ONE LINE DIAGRAM

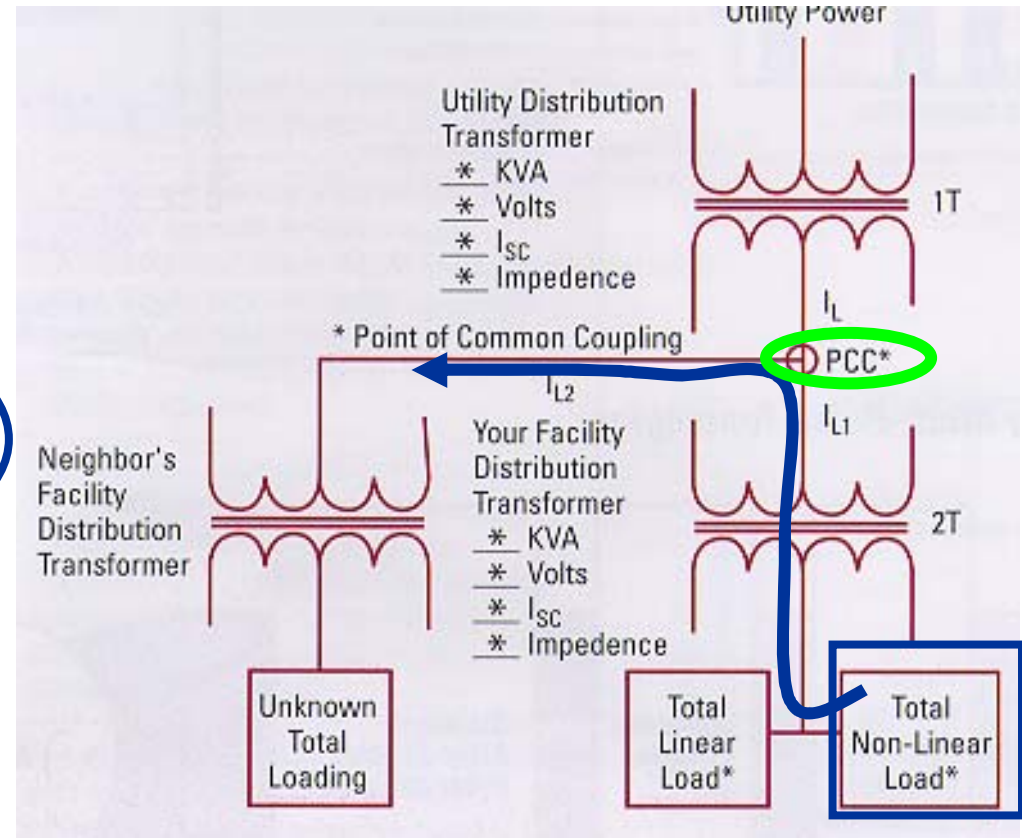

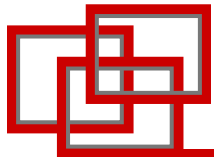


Who is your neighbor?

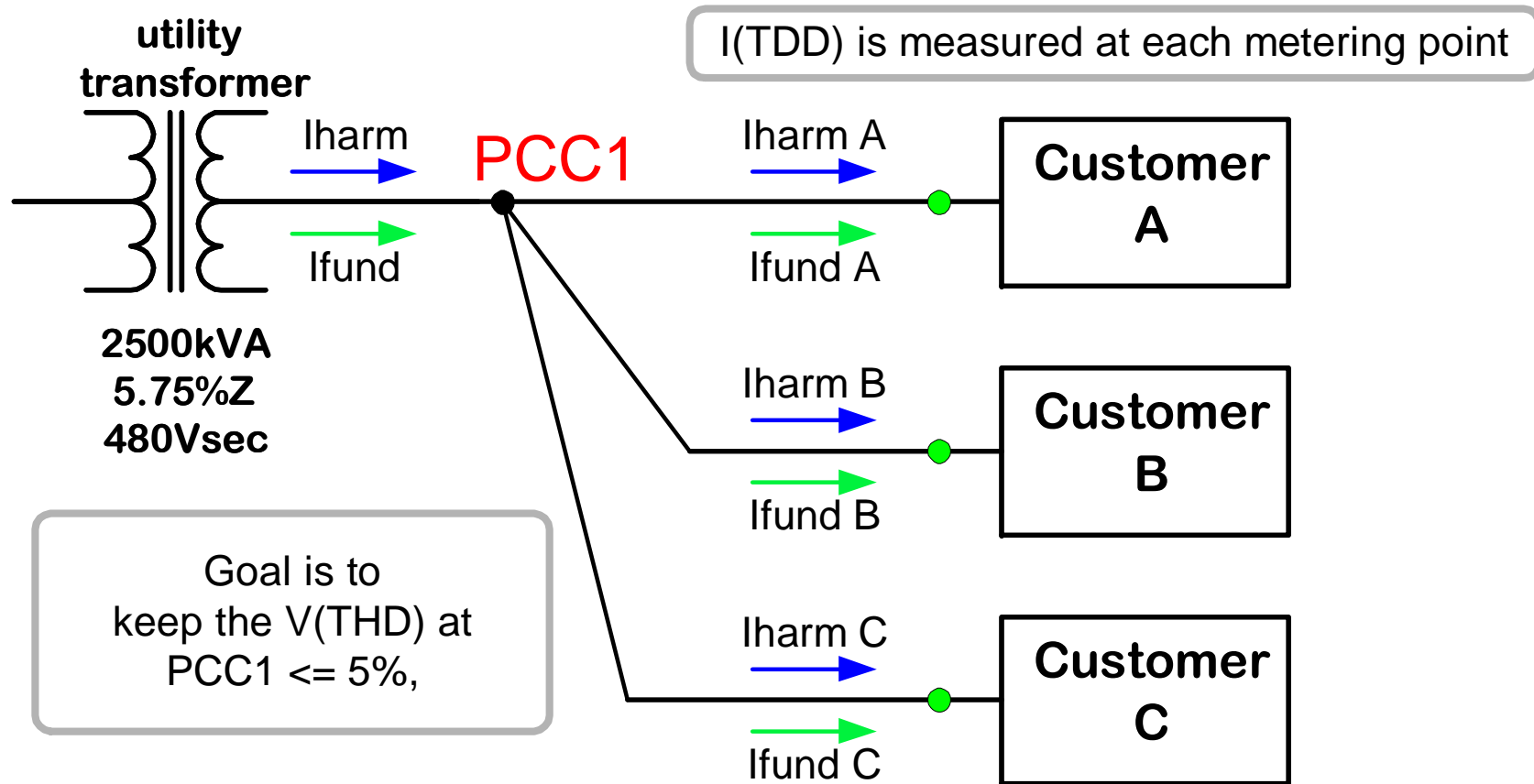

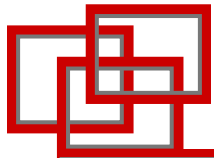

How to Tackle Harmonics?


- It is not economical or desirable to eliminate all harmonics
- Analysis & guidelines are necessary to determine whether or not there are problems created by existing harmonics
- Useful Guidelines & Standards available are:
 - IEEE- 519 is the Main Standard in North America
 - (places limits on voltage distortion & current THD)
 - IEC- 555 for Europe & some areas of South America
 - (places limits on voltage distortion)
 - IEC- 61000-3-12 proposed draft
 - (places limits on voltage distortion for input current $>16A$ and $< 75A$)

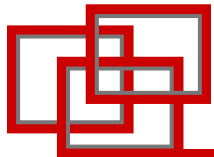


Harmonic Distortion Limits of IEEE-519

- Developed by utilities, electrical equipment manufacturers and power consumers
- Recommended Harmonic Limits are based on reasonable voltage distortion limits at (PCC)
 - PCC is where two or more customers share a common utility power source
- Distortion is Relative to the total plant load
 - i.e. each plant's harmonic limit is different
- Specification Harmonic Limits increasingly common in low voltage systems

PLANT ONE LINE DIAGRAM

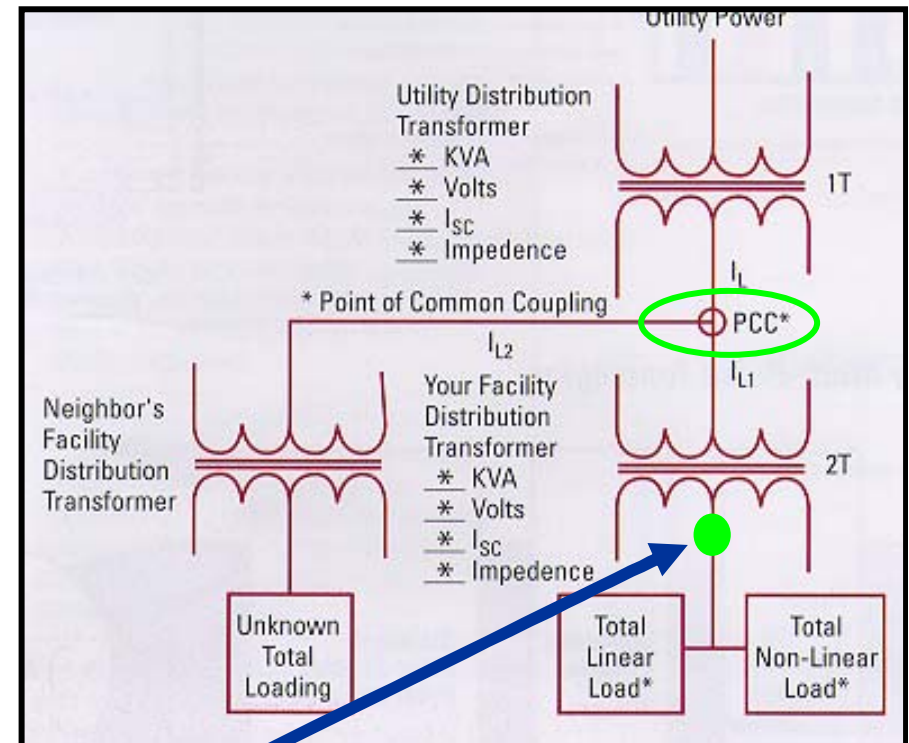

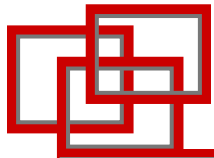


Voltage Distortion Limits of IEEE-519

Harmonic Voltage Distortion at PCC in %

	< 6.9 kV	6.9 kV- 13.8 kV	> 13.8 kV
Maximum individual harmonic component	3.0 %	1.5 %	1.0 %
V_{THD}	5.0 %	2.5 %	1.5 %



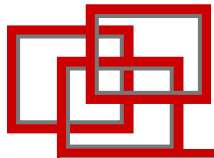

- IEEE 519 Harmonic Standard for power systems has:
 - ⇒ GENERAL limit set at 5% THD
 - ⇒ HOSPITAL , AIRPORT limit set at 3% THD




Current Distortion Limits of IEEE-519

Maximum Harmonic Current Distortion in % of Fundamental

I_{sc} / I_L	$h < 11$	$11 < h < 17$	$17 < h < 23$	$23 < h < 35$	THD

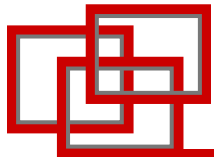- I_{sc}  system short circuit current at PCC.
- I_L  maximum load demand at PCC.
- THD  Total Harmonic Current Distortion allowed at PCC.
- Higher (I_{sc} / I_L)  measure of power system "stiffness"




Current Distortion Limits of IEEE-519

Maximum Harmonic Current Distortion in % of Fundamental

Isc / IL	h < 11	11 < h < 17	17 < h < 23	23 < h < 35	THD
< 20	4.0	2.0	1.5	0.6	5.0
20 - 50	7.0	3.5	2.5	1.0	8.0
50 - 100	10.0	4.5	4.0	1.5	12.0

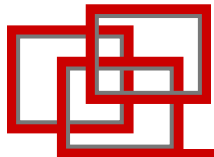- Higher (Isc / IL) ⇒ “stiff” power system ⇒ more THD allowed
- Designing a system with a strong power source diminishes the impact of harmonics. If a back-up generator is utilized, this should also be taken into consideration.




Current Distortion Limits of IEEE-519

Maximum Harmonic Current Distortion in % of Fundamental

Isc / I_L	h < 11	11 < h < 17	17 < h < 23	23 < h < 35	THD
< 20	4.0	2.0	1.5	0.6	5.0
20 - 50	7.0	3.5	2.5	1.0	8.0
50 - 100	10.0	4.5	4.0	1.5	12.0

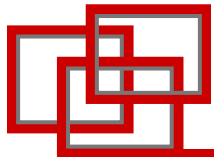
- Worst Case Application of IEEE - 519 \Rightarrow (Isc / IL) < 20 Category



What are the IEEE 519-1992 standards?


Harmonic Voltage Limits		Table 10.2
Low-Voltage Systems		
Application	Maximum THD (%)	
Special Applications - hospitals and airports	3.0%	
General System	5.0%	
Dedicated System - exclusively converter load	10.0%	

Current distortion Limits for General Distribution Systems (120V through 69,000V)						
Maximum Harmonic Current Distortion in Percent of Iload						
Isc/Iload	<11	11<=h<17	17<=h<23	23<=h<35	35<=h	TDD (%)
<20	4.0	2.0	1.5	0.6	0.3	5.0
20<50	7.0	3.5	2.5	1.0	0.5	8.0
50<100	10.0	4.5	4.0	1.5	0.7	12.0
100<1000	12.0	5.5	5.0	2.0	1.0	15.0
>1000	15.0	7.0	6.0	2.5	1.4	20.0
Even harmonics are limited to 25% of the odd harmonic limits above						
						Table 10.3
Isc=maximum short circuit current at PCC						
Iload=maximum demand load current (fundamental frequency component) at PCC						

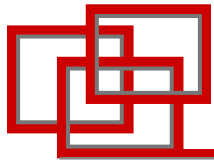


Harmonic Mitigation Techniques

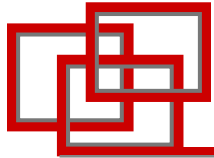When **Non-Linear Loads exceed 30% - 50%** of Total Load,
an harmonic analysis of the plant one-line load
diagram should be performed.




How can we reduce the harmonic current?

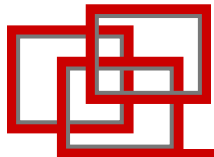- DC link choke within the drive
- line reactor
- passive filter
- active filter
- multi-pulse converters
- active front-end




Input Current of 6-Pulse Rectifier

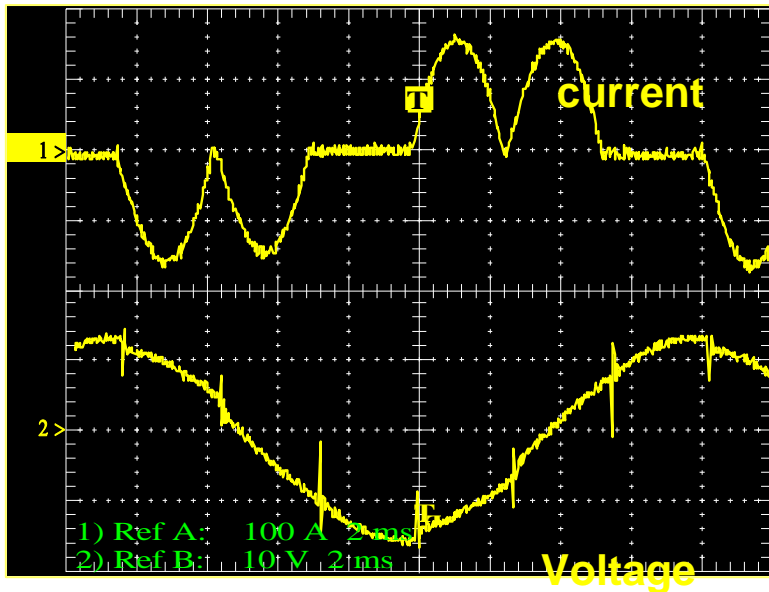


Standard Configuration - "no" DC link Choke

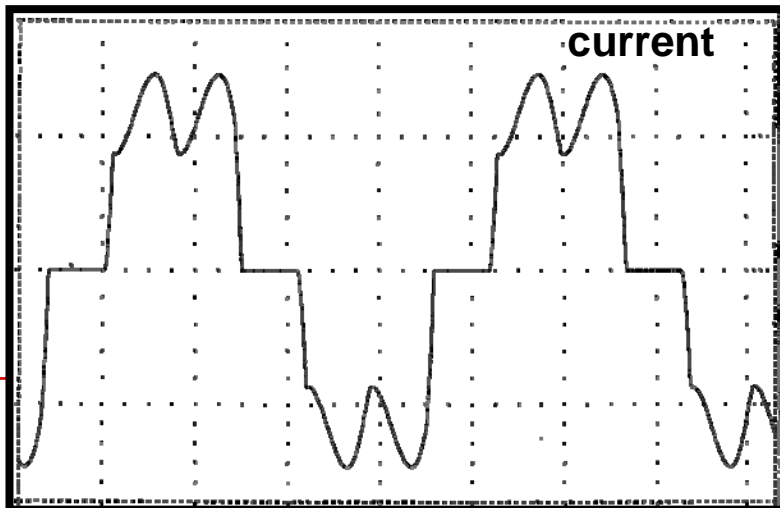- Current THD= 80% @ full load
- THD depends on source impedance(%Z)
- Rectifier diode turn off causes voltage spikes on voltage waveform
- For Single drives < 5 HP, low impact on utility




Standard Configuration - "with" DC link Choke

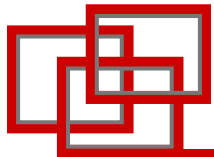- Current THD= 32% @ full load
- THD independent of source %Z
- Good power factor = 0.93
- Minimizes input voltage distortion




Drive w/o DC Link Choke

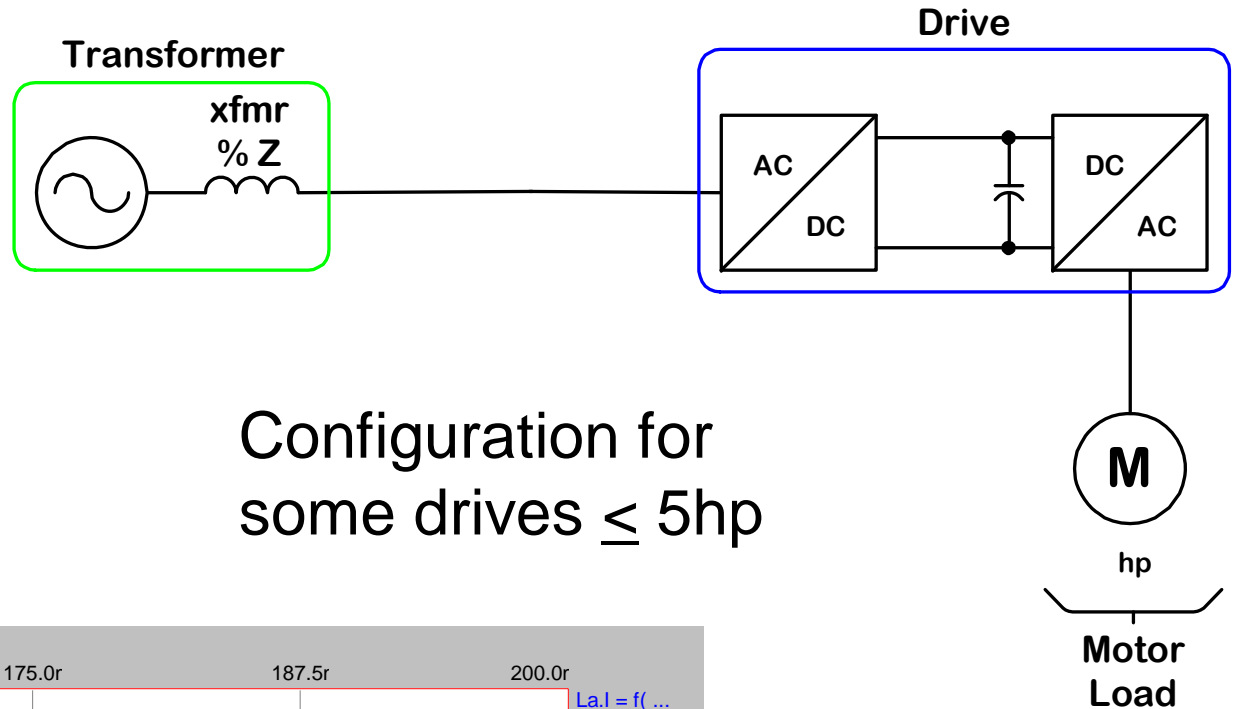
- Typical I(THD) of 80 to 120%
- Sensitive to line voltage transients
- High peak line currents



Configuration for
some drives ≤ 5 hp


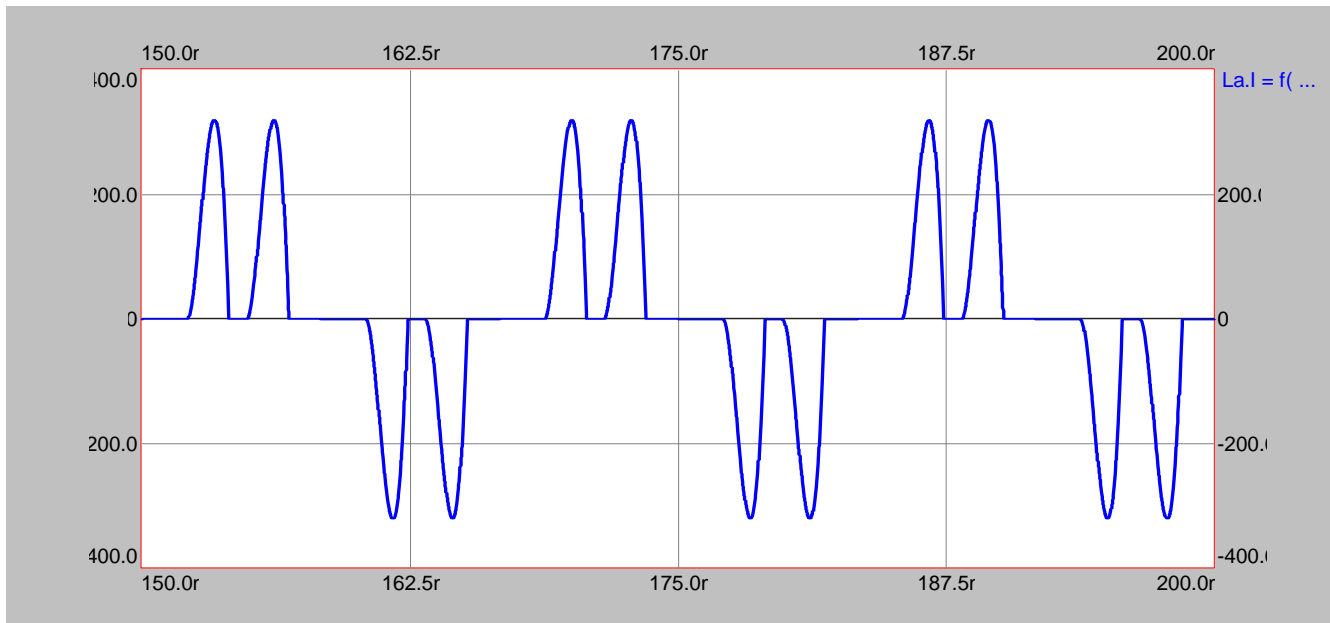


NOTE: I_{pk} about $3 \times I_{rms}$

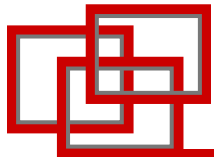


Drive with DC Link Choke

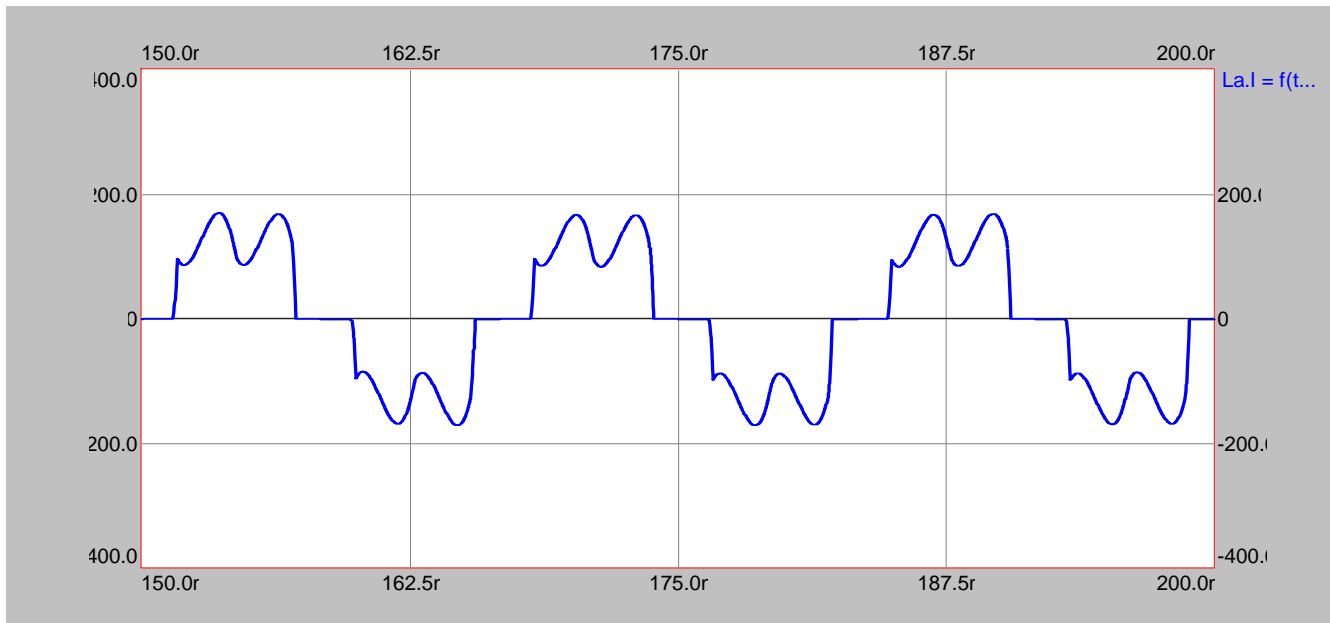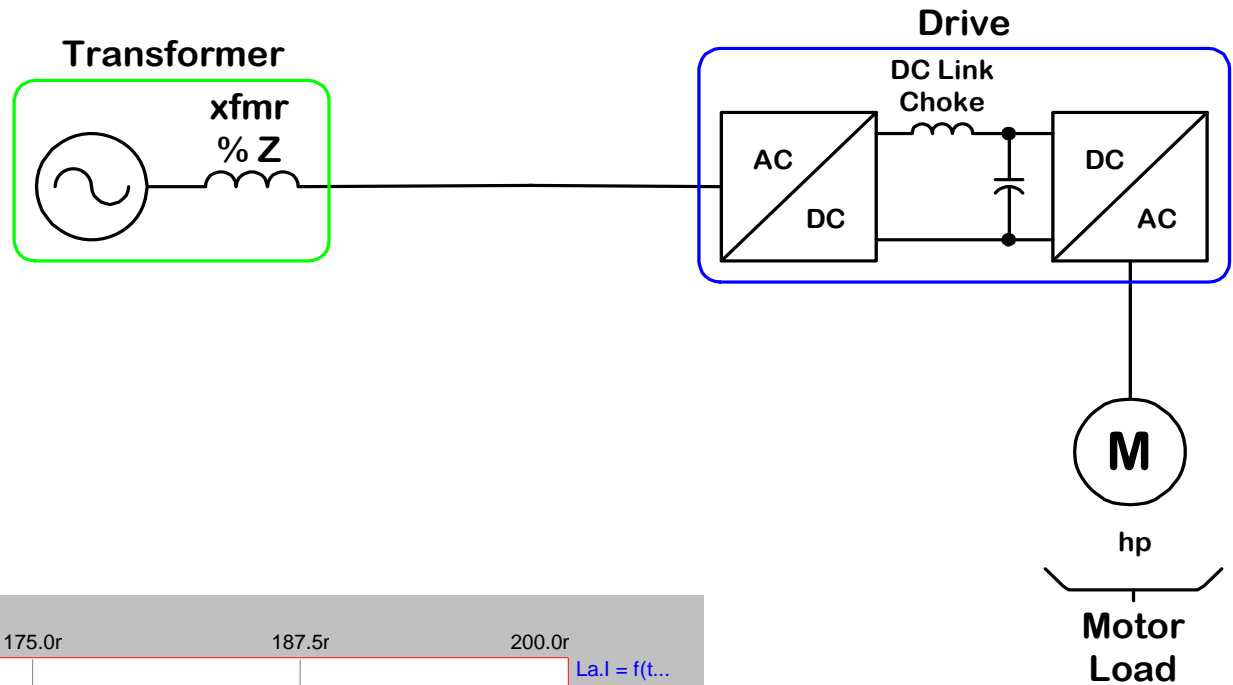- Typical I(THD) of 30 to 40%
- Less sensitive to line transients




NOTE: I_{pk} about 1.5x I_{rms}

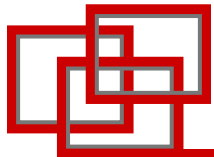


Line Reactor, Drive w/o DC Link Choke

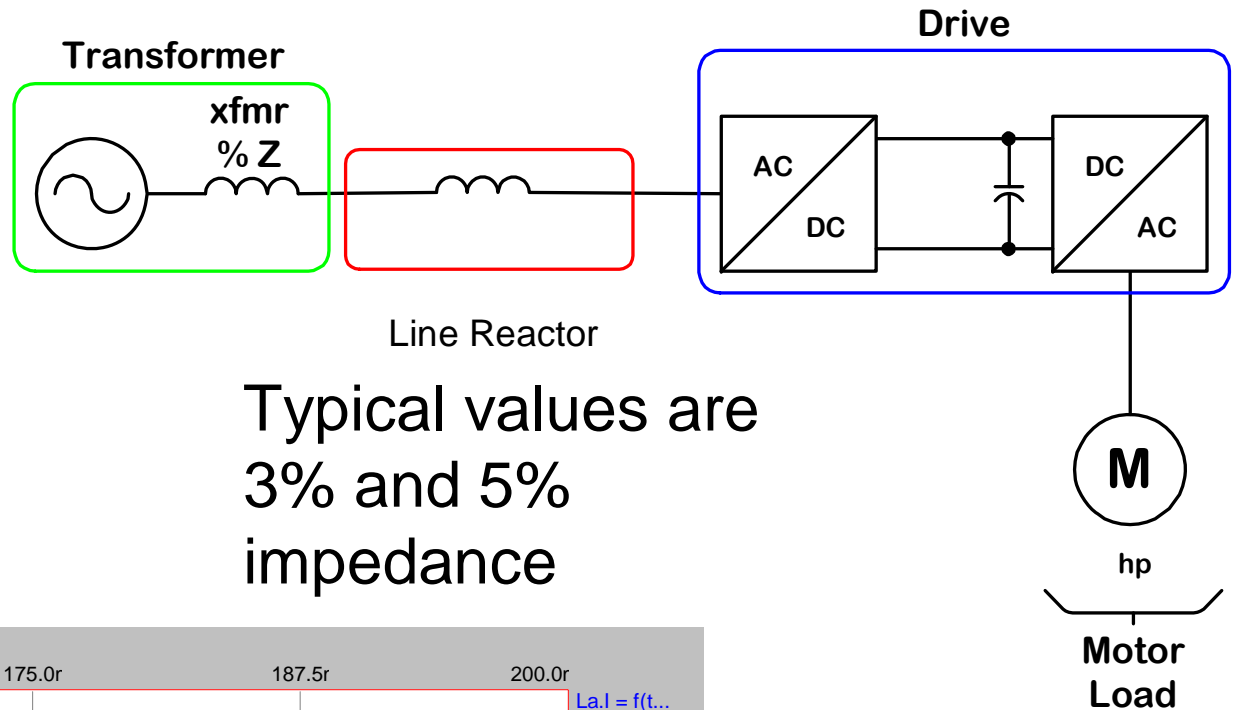- Typical I(THD) of 30 to 45%
- Big help for drives without DC link choke




Typical values are
3% and 5%
impedance

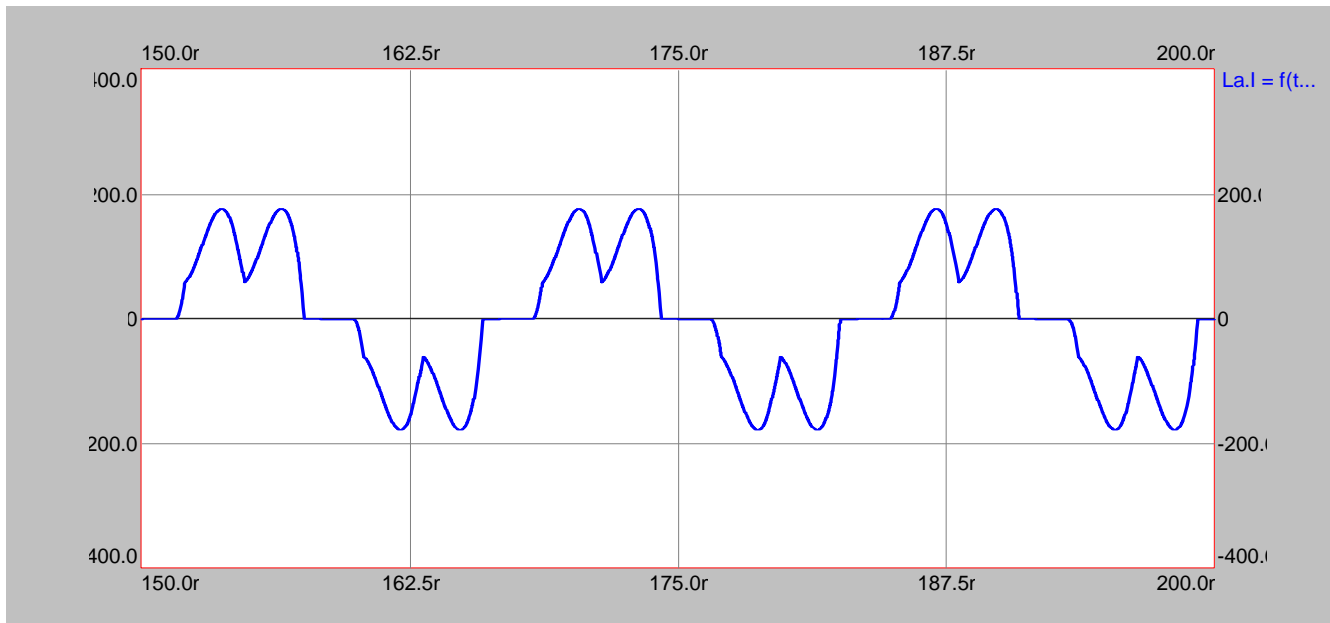


NOTE: shown is 3% LR

Line Reactor

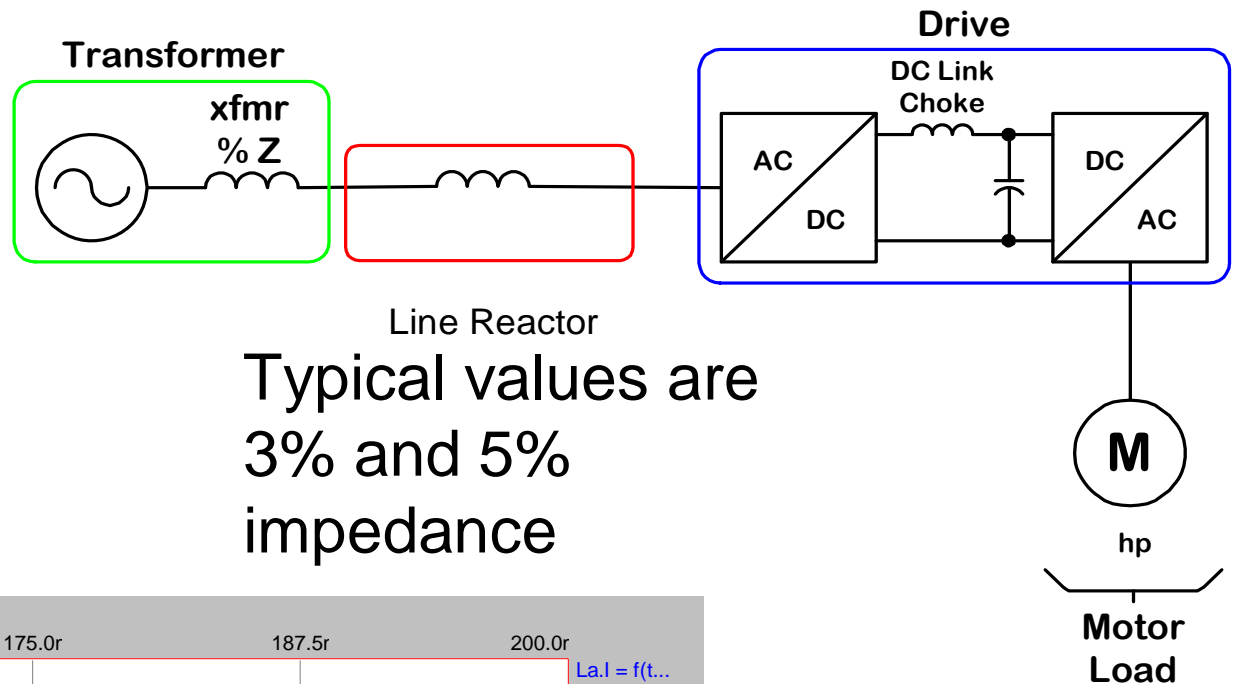
- Typical I(THD) of 20 to 35%
- Big help for drives without DC link choke



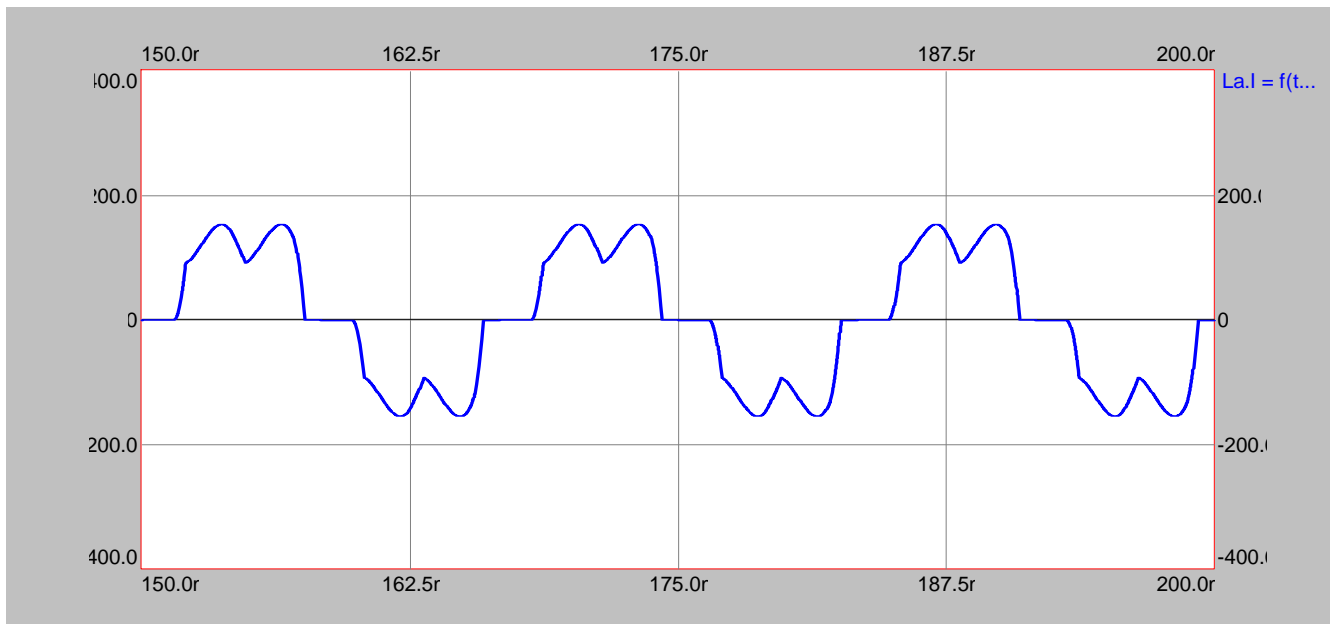Line Reactor
 Typical values are
 3% and 5%
 impedance



NOTE: shown is 3% LR

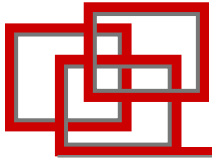

Harmonic Mitigation Technique - Passive & Active Filters


Passive Filters:

**eliminate/reduce specific harmonics (tuned 5th, 7th filters)
reduce higher order harmonics (low pass, 5th thru 17th)**

Active Filters:



**using switching converters to compensate for specific harmonics and/or improve Power Factor
It injects equal and opposite of Drive harmonics into AC line**

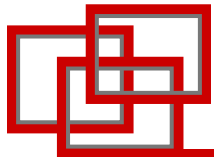
Let's, look at these solutions in more detail !




Passive Harmonic Filter


- Typical I(THD) of 5 to 8%

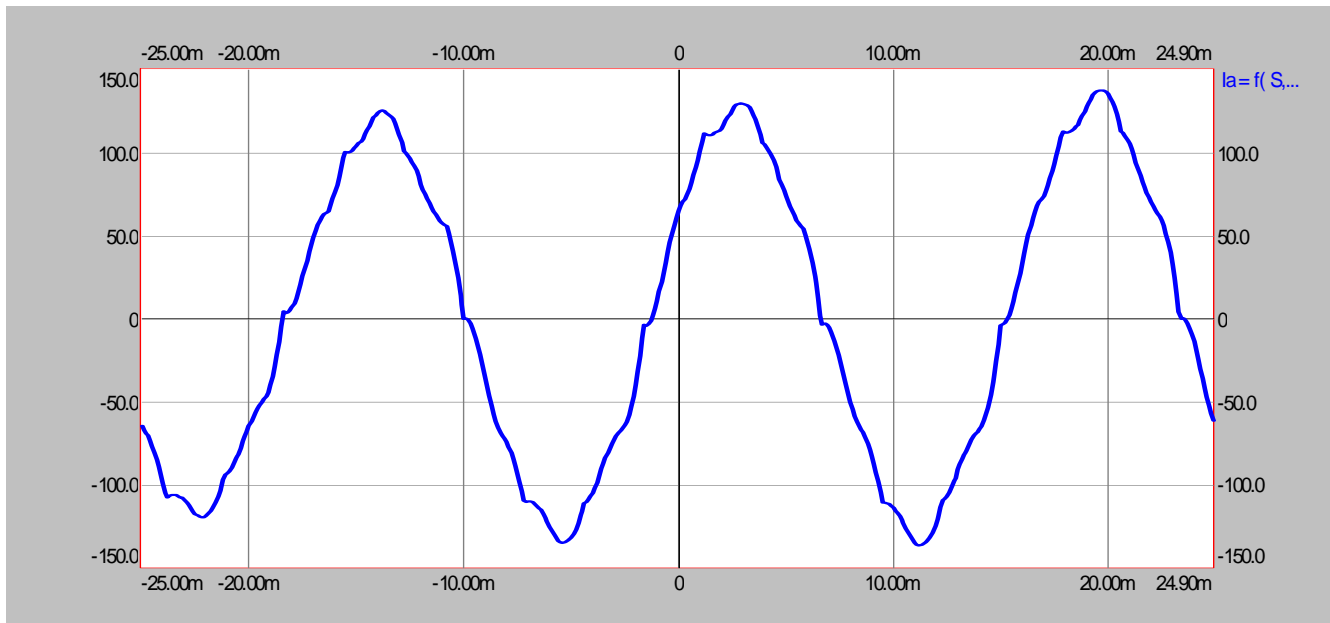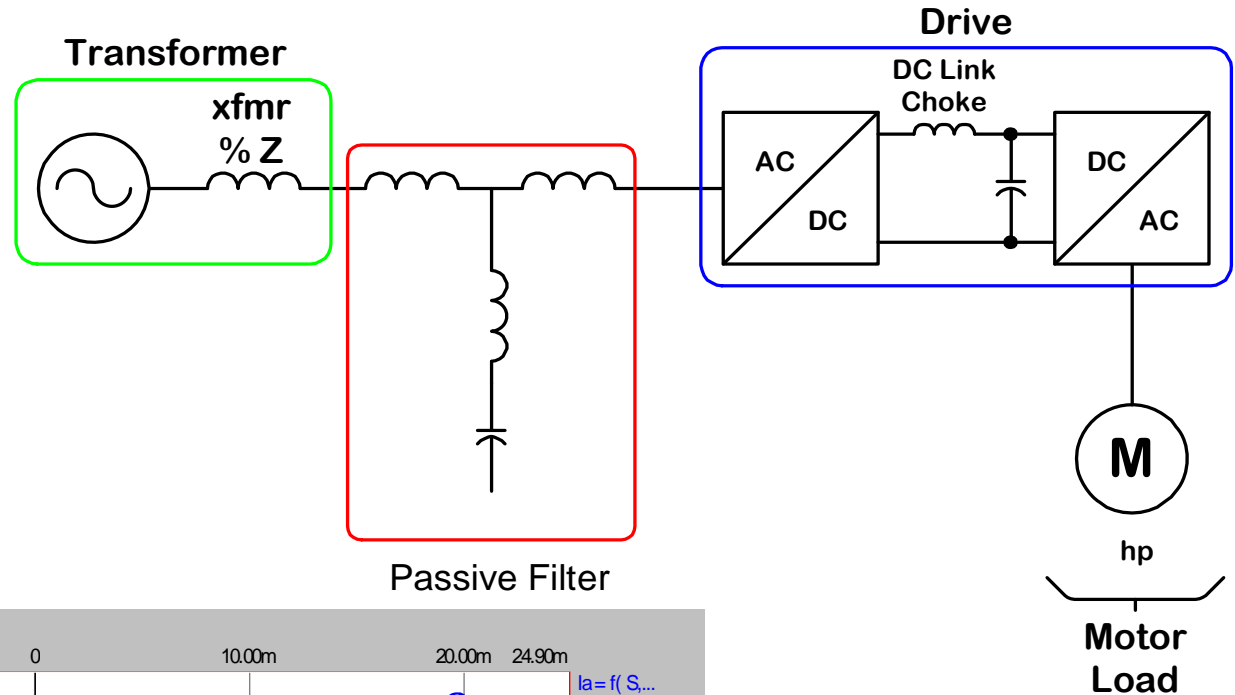

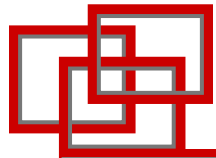



Passive Harmonic Filter

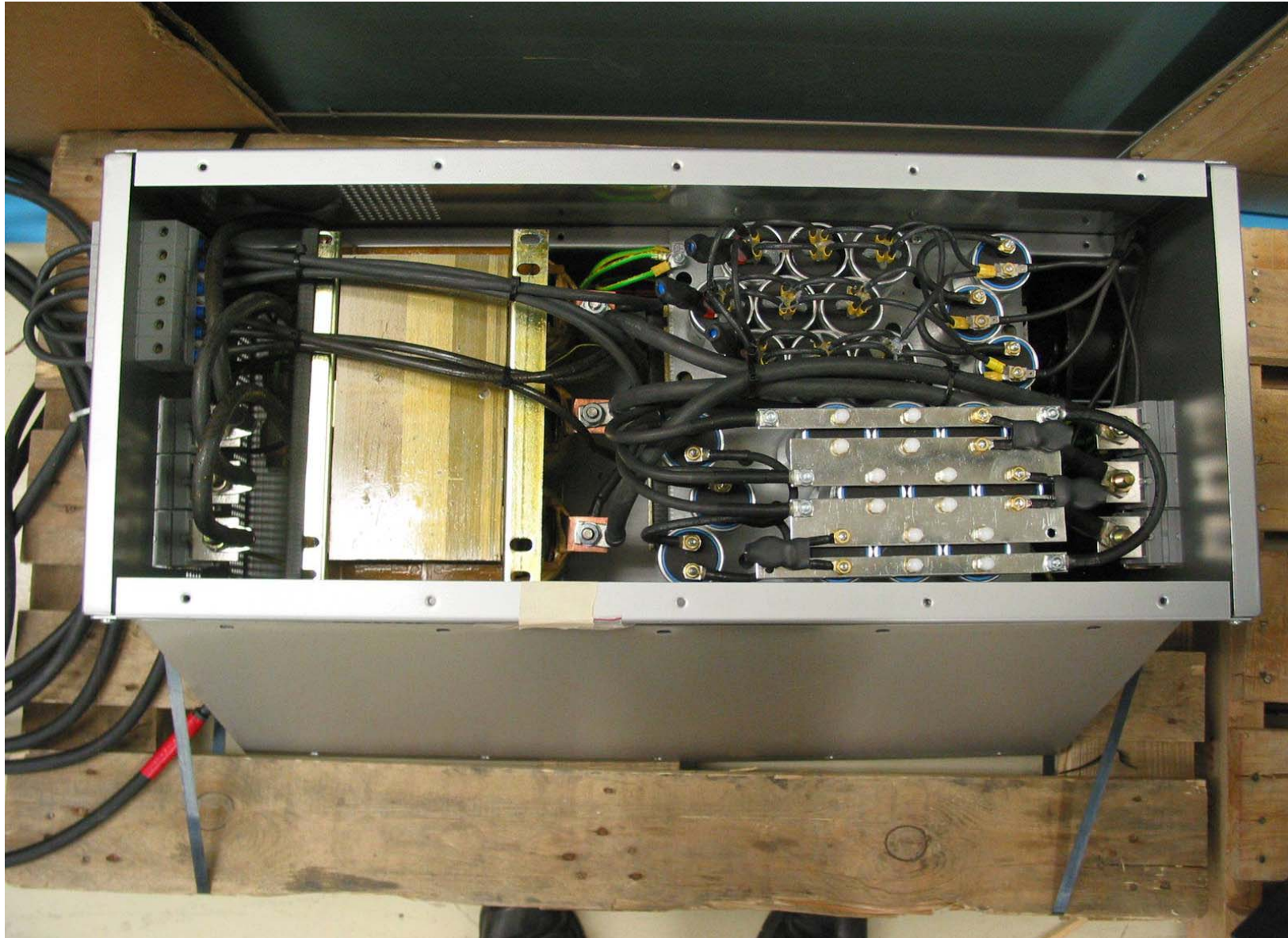


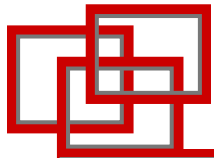

Passive Harmonic Filter - Dual


- Typical I(THD) of 4 to 7%

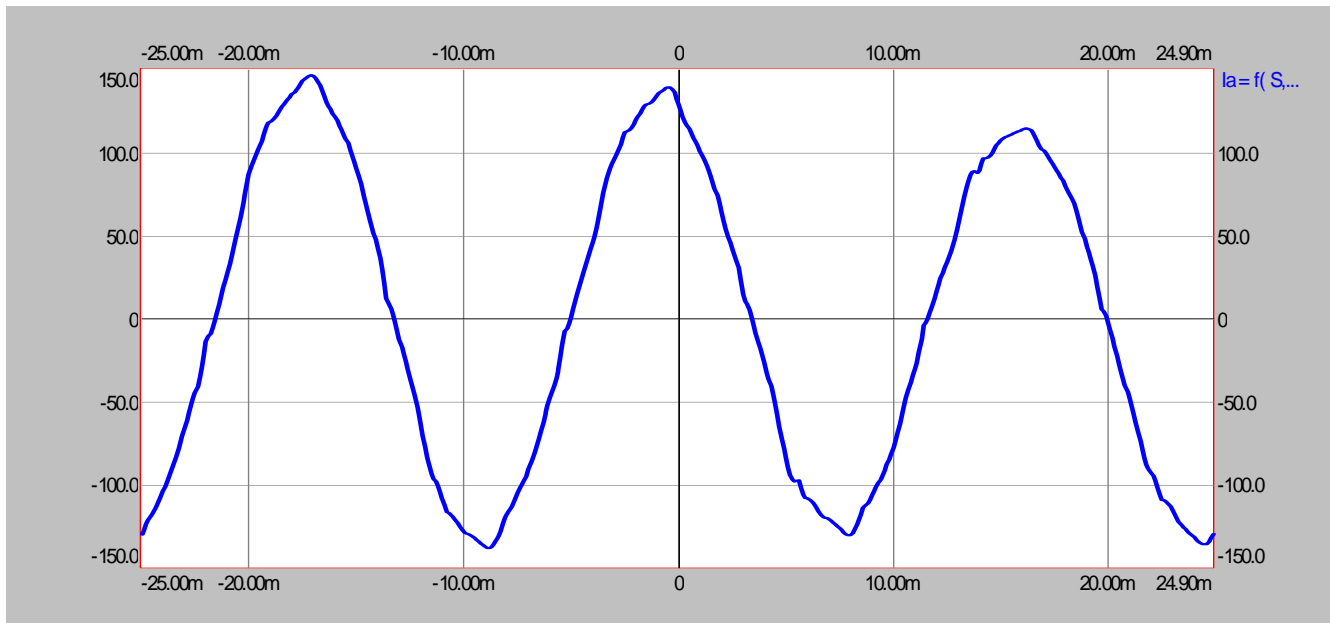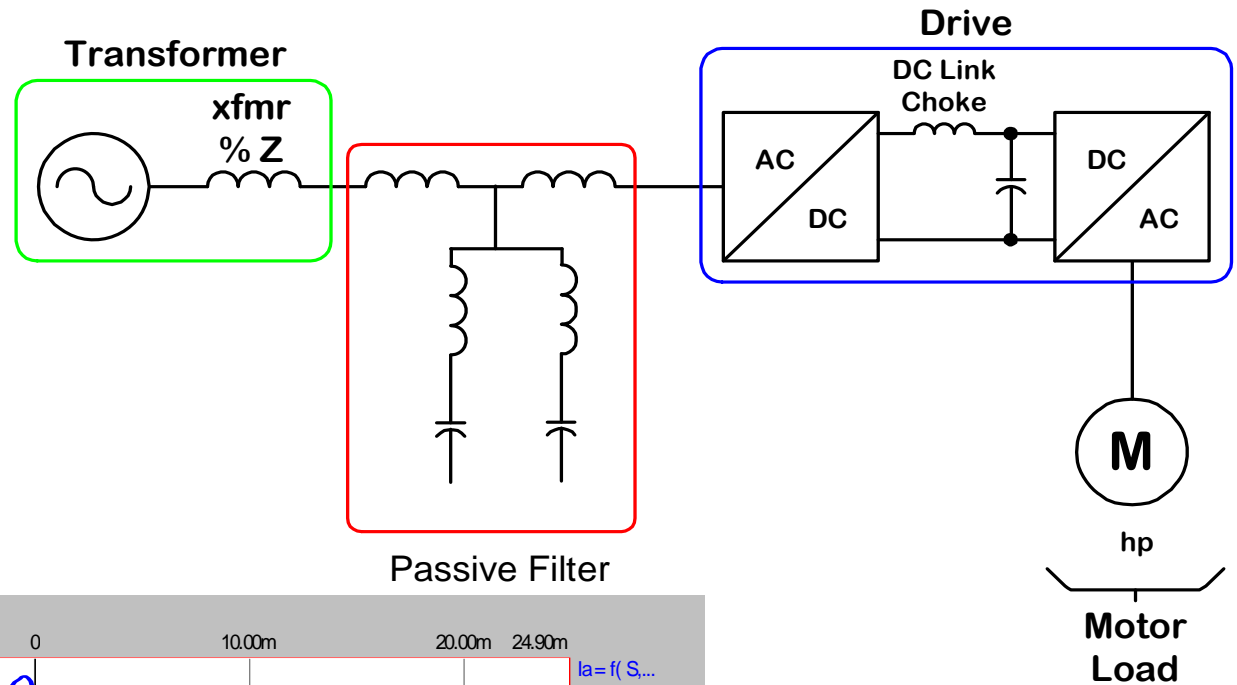

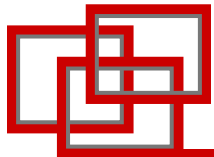


Passive Filter: Harmonic Trap Filter

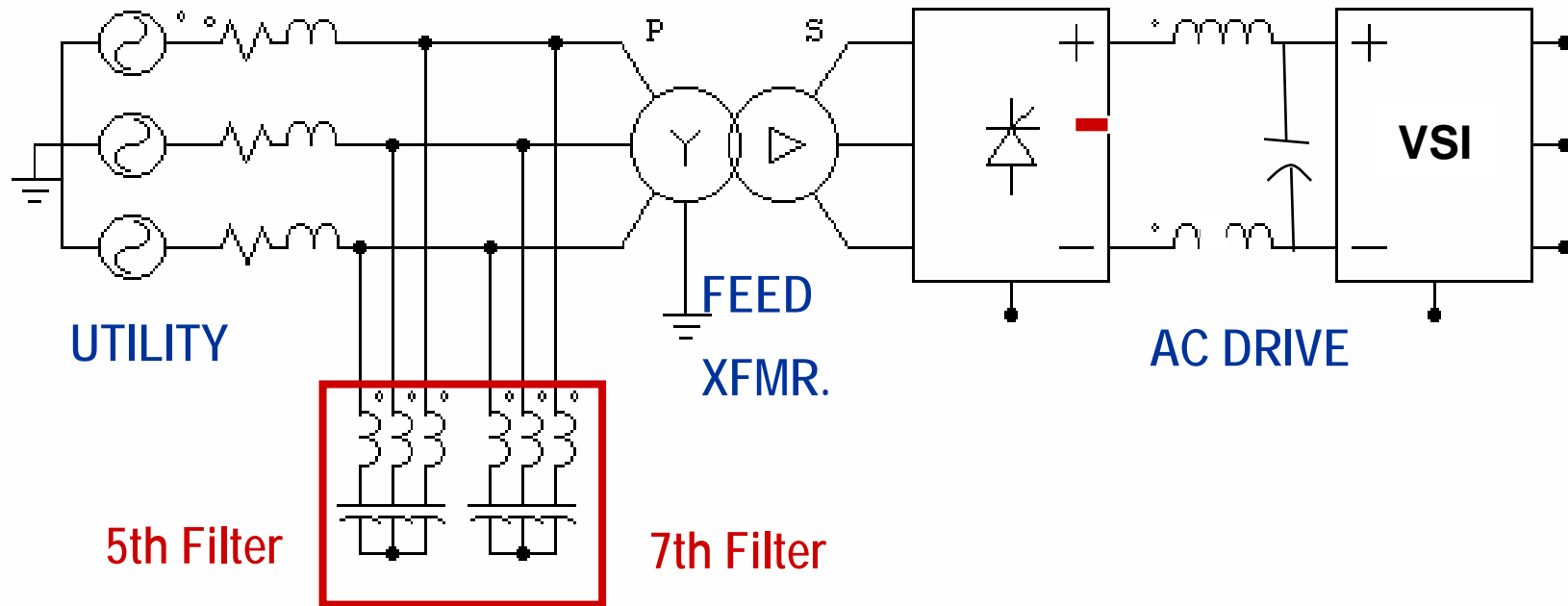
6-pulse rectifier with tuned 5th & 7th filter



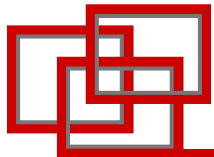
Consists of one or more tuned 5th or 7th LC filters in shunt with power system. Usually connected at the primary of the isolation transformer or line reactor. Filters interact with other plant non-linear loads, can sink for unknown load. Need overload and fuse blown detection (usually individually fused).



Active Filter Concept

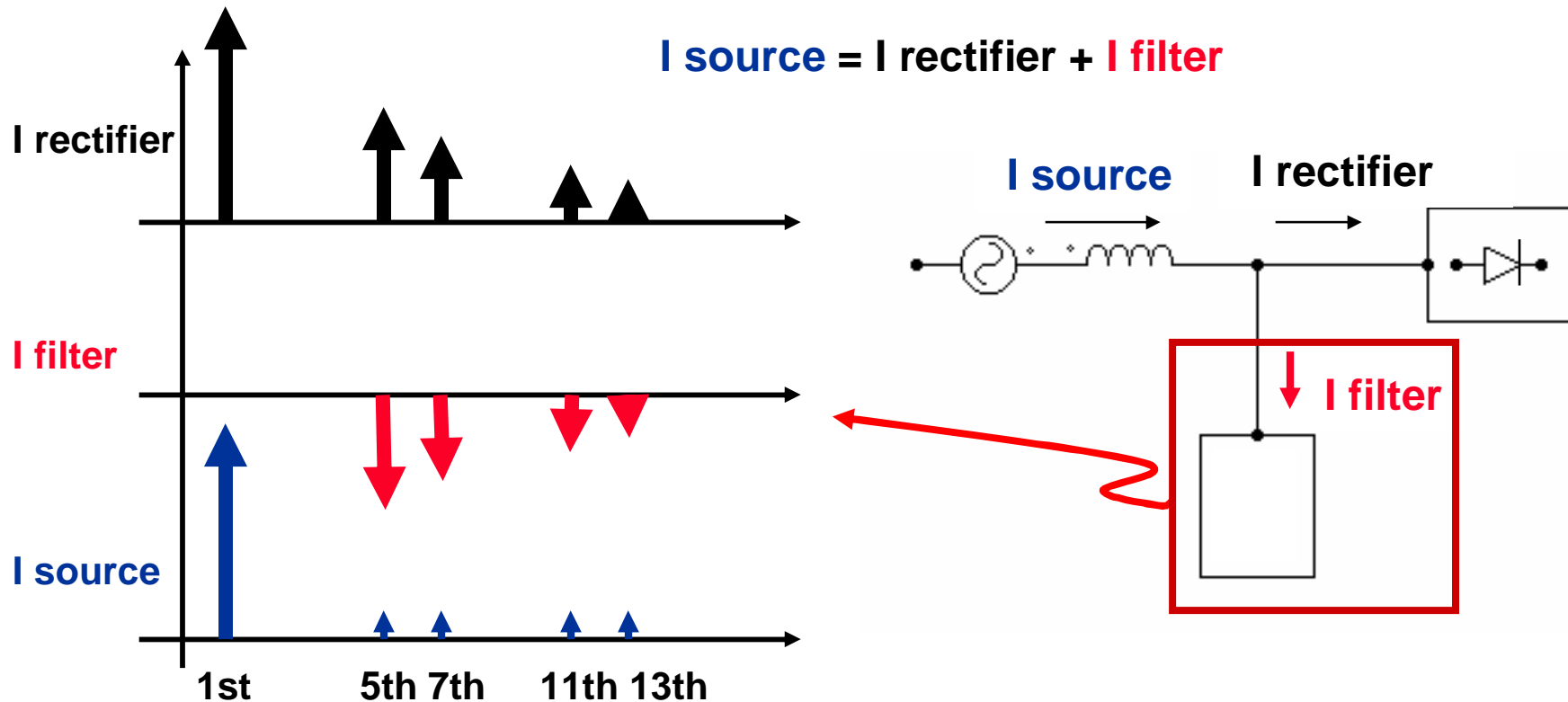


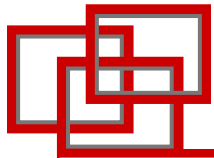- High Filter Converter ratings: ~ 1/3 of Drive kVA
- Multi-functional: reactive power factor compensation, voltage and load balancing





Active Harmonic Filter

- Typical I(THD) of 3 to 6%

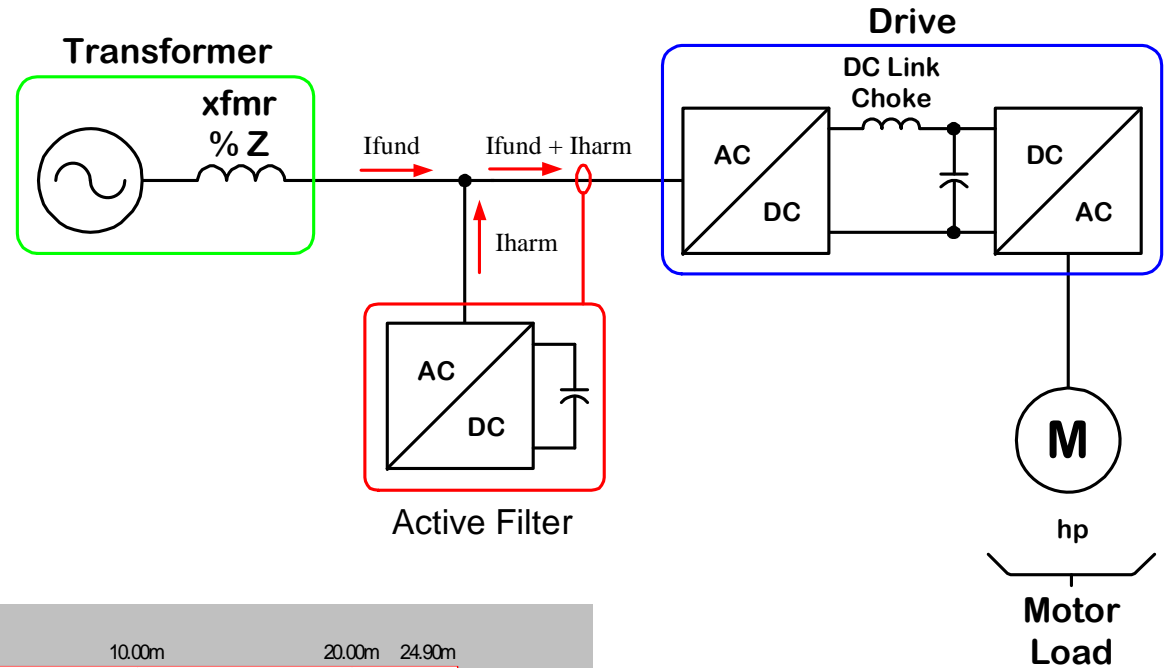



Current from Transformer

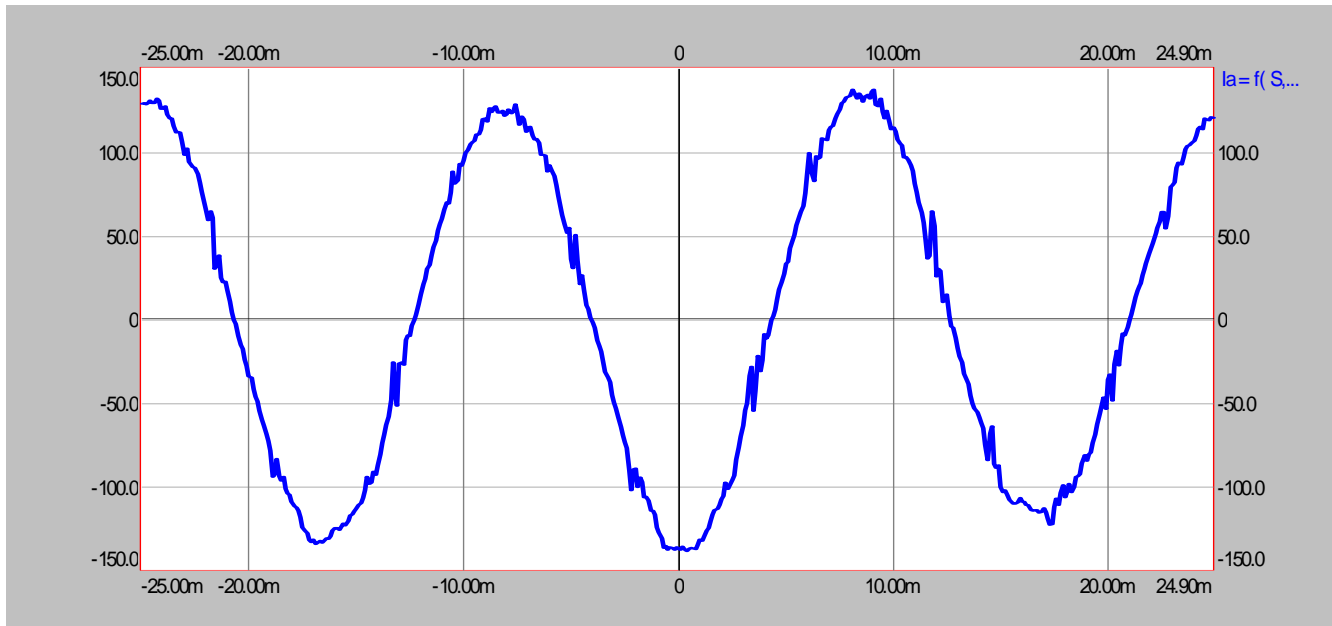

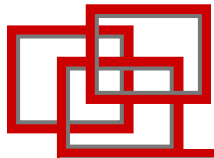



Active Harmonic Filter

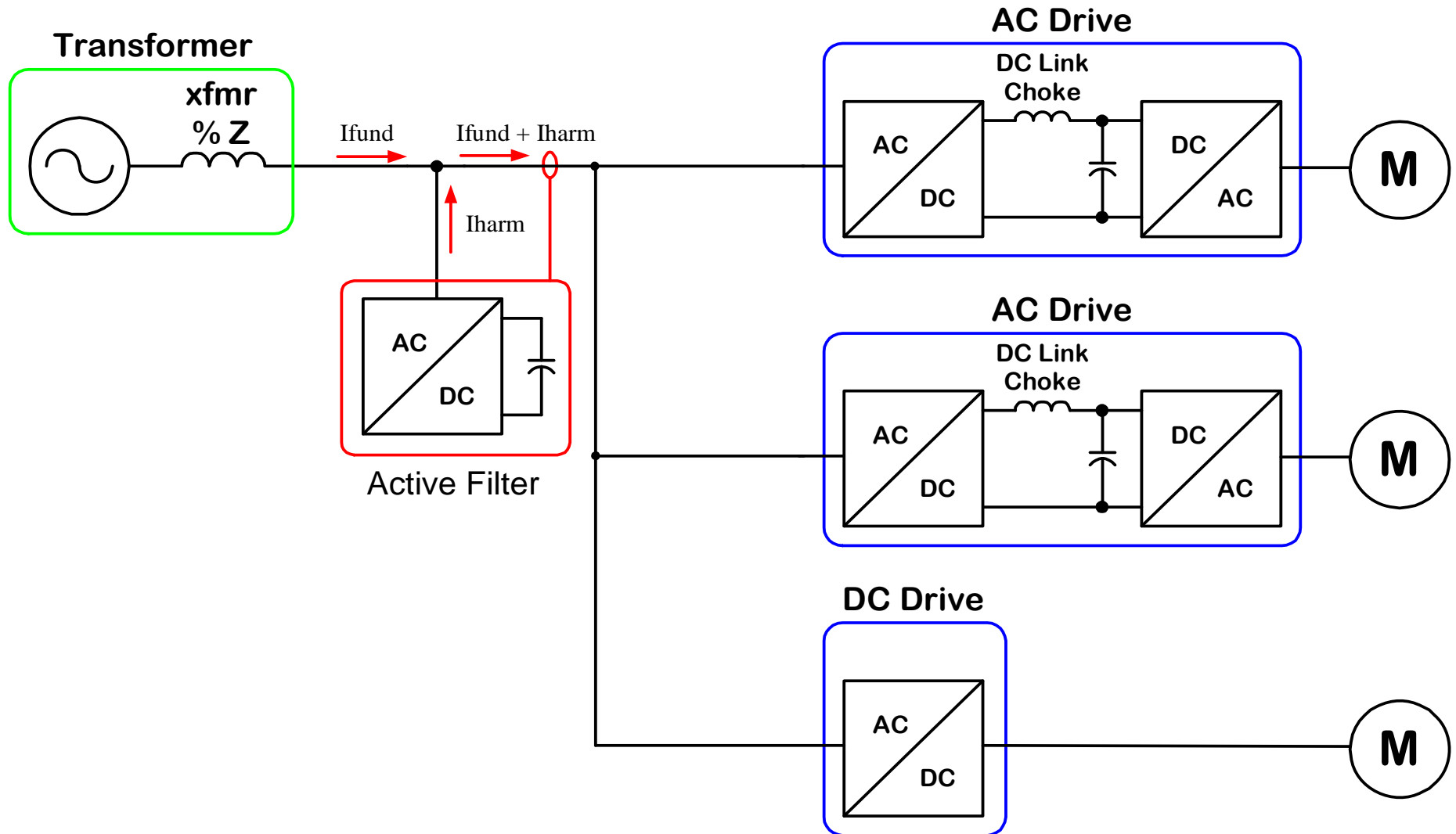

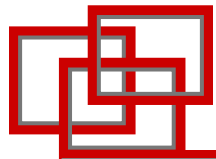


Active Harmonic Filter

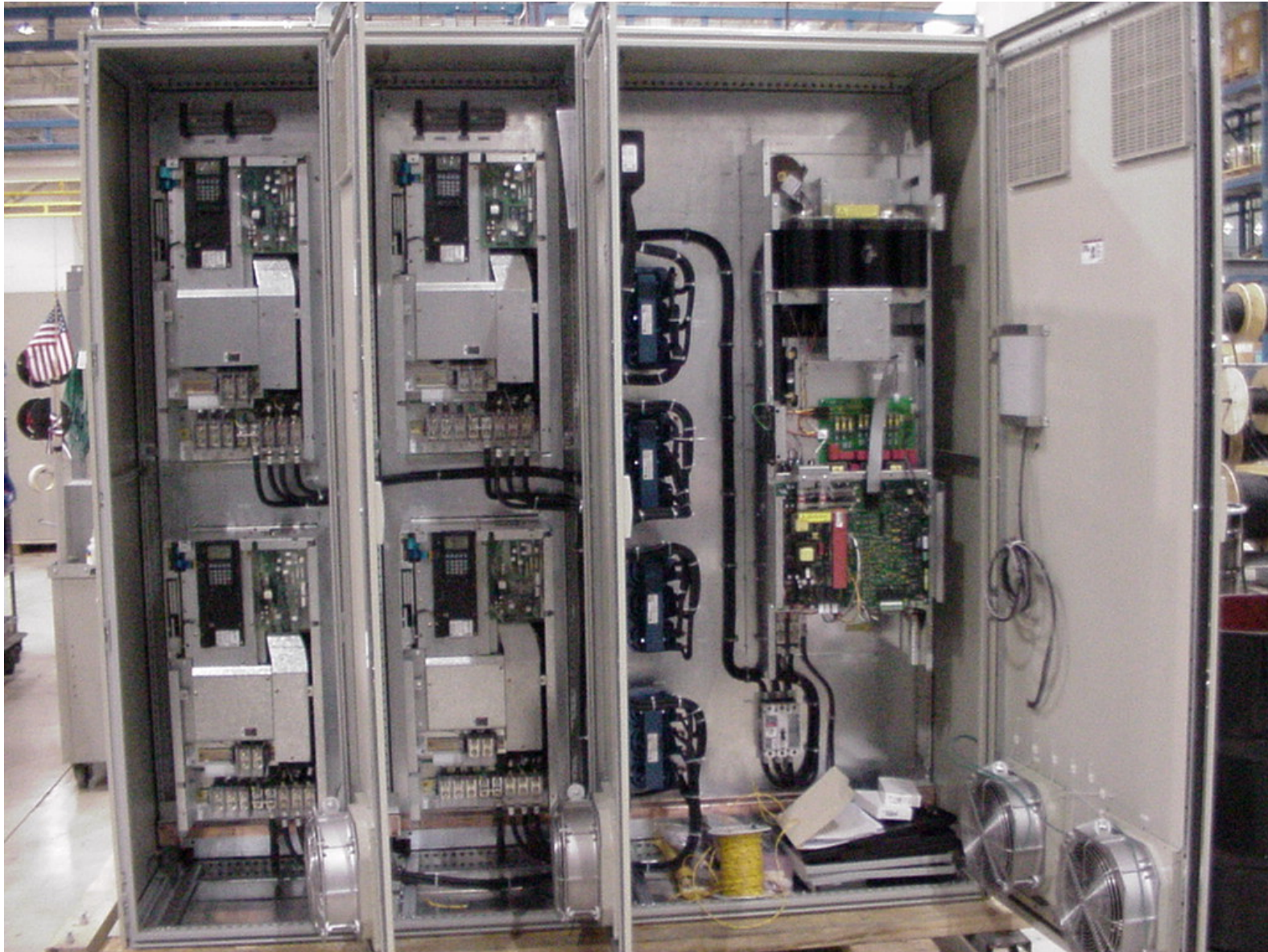


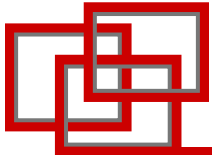

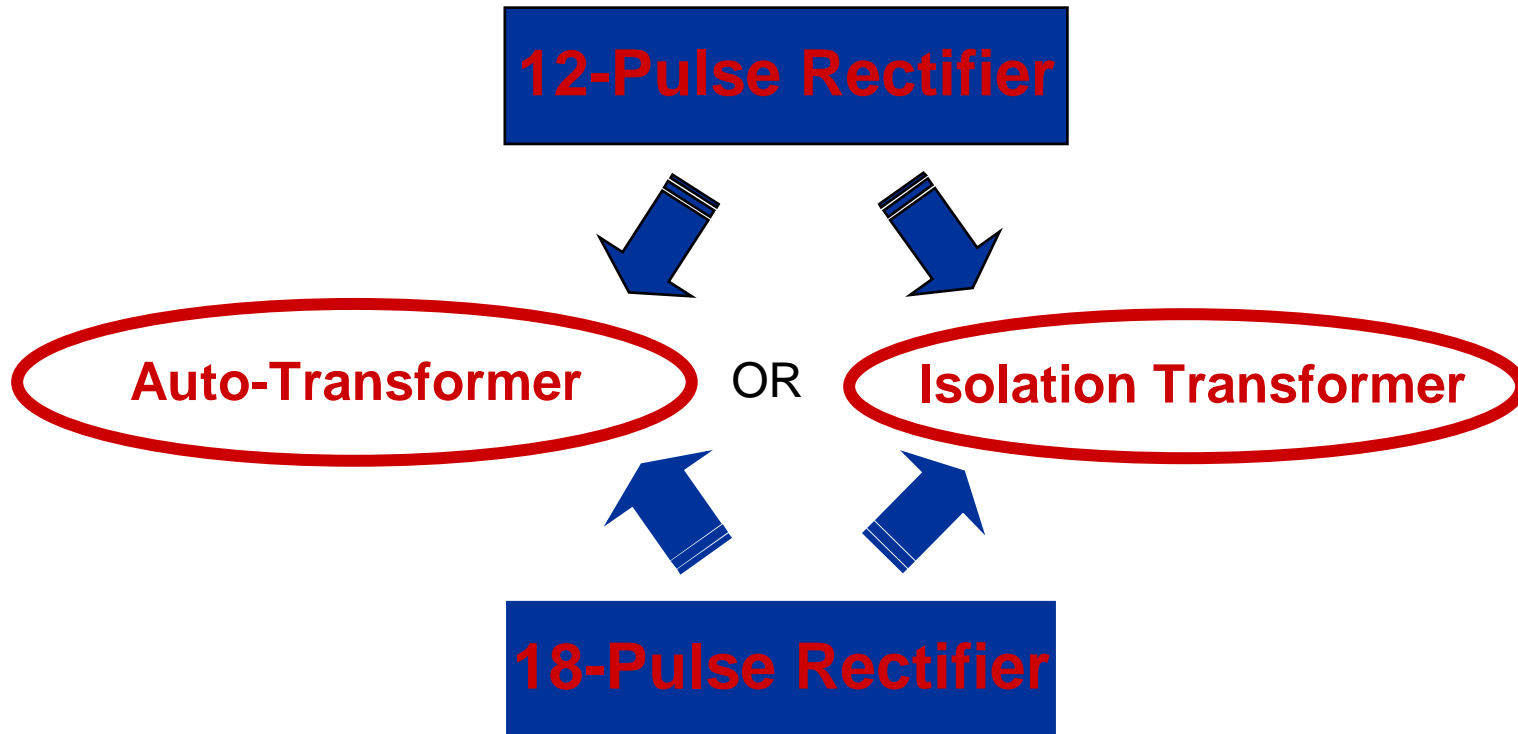Harmonic Mitigation Technique Rectifier's with Higher Pulse Number





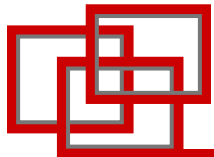
- 18-pulse drives produce less THD, but are larger & more expensive
- Isolation transformers produce less THD, but larger & more expensive




Multi-Pulse Converters

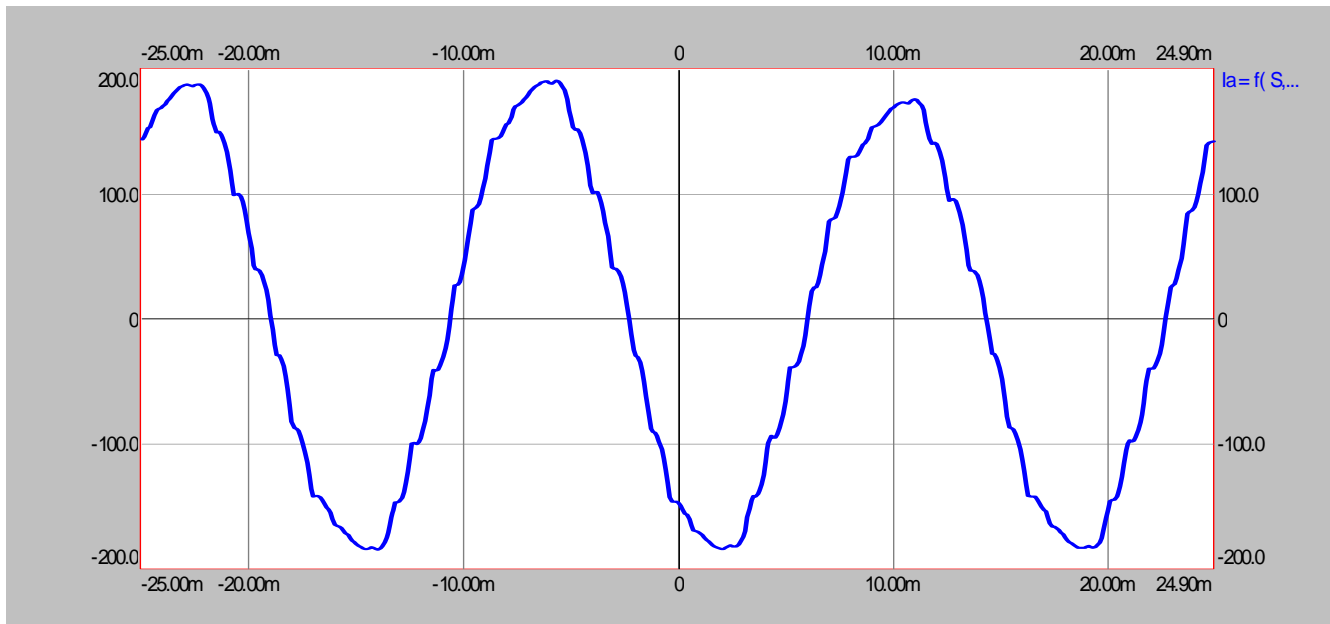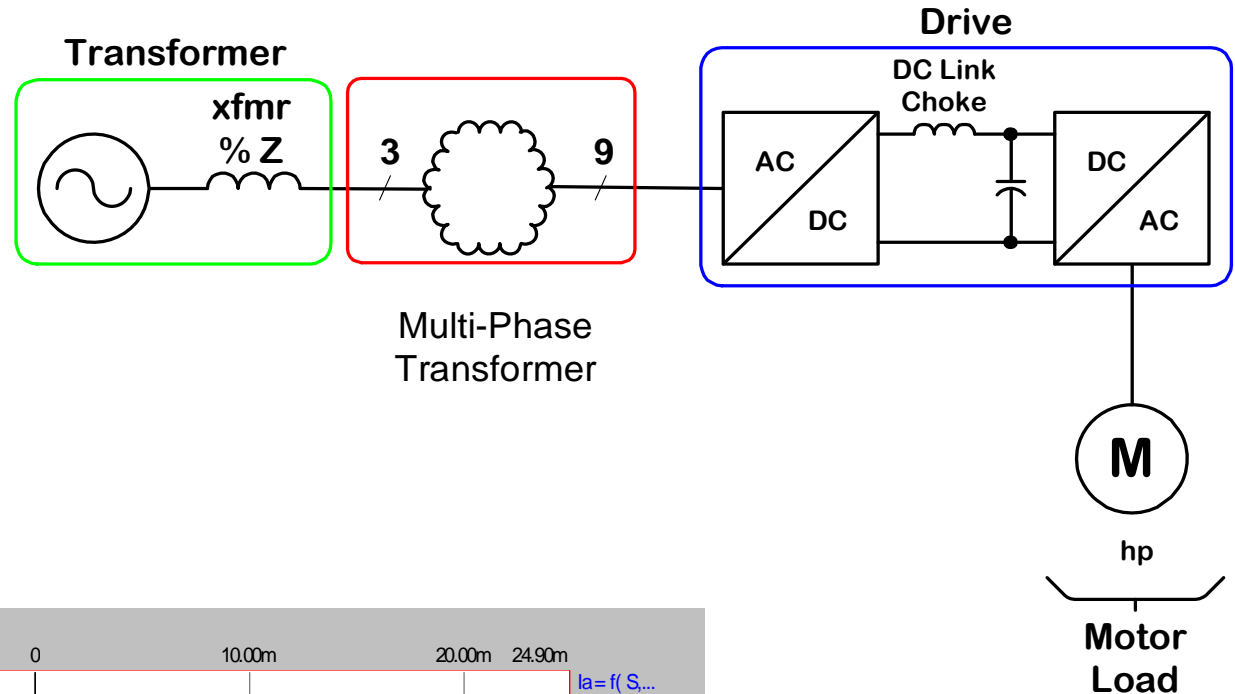- 12-Pulse Typical I(THD) of 9 to 12%
- 18-Pulse Typical I(THD) of 4 to 5%




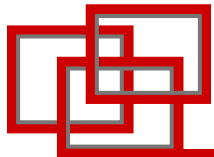

18-Pulse, Parallel

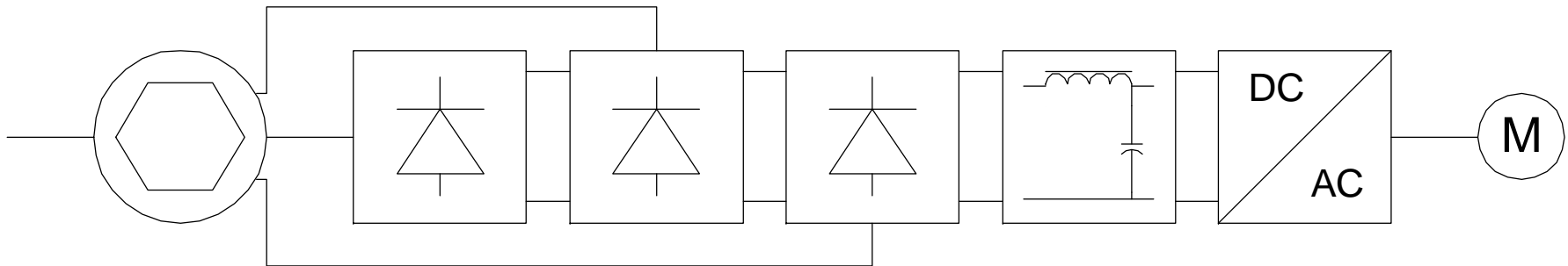

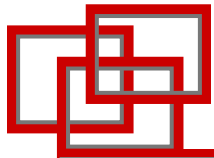- Auto-transformer with polygon windings (480V primary for 480V drive)
 - 1/3 the size of the isolation xfmr
 - Can have isolated primary - larger
- Diode bridges are in parallel – one third current rating
- 9 wires from transformer to bridges
- $I(\text{THD}) = 3 \text{ to } 5\%$




18-Pulse Auto-Transformer Converter

Supply Transformer


Line Reactor

Auto-Transformer

18 Diode Bridge

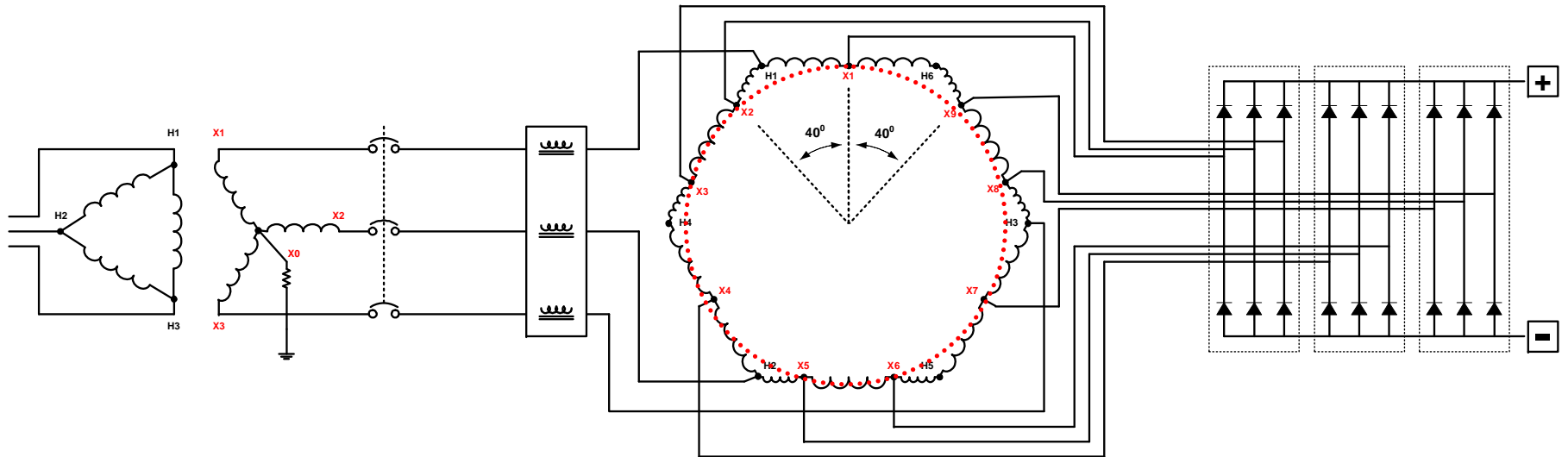


NOTE: 5 windings per core leg

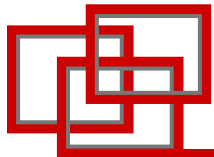


Input Waveforms of 18-Pulse Option

FEATURES

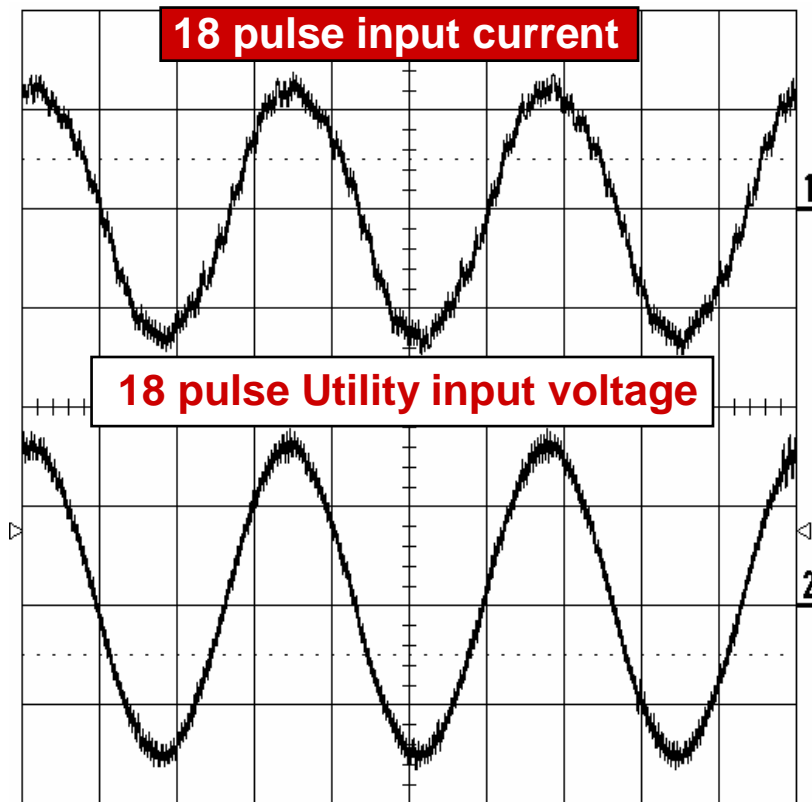


- Meets IEEE-519 5% Harmonic Standard at the drive input Terminal
- Current THD 3.5% full load (typ.), 6 % no load
- 5th, 7th, 11th & 13th harmonic reduced
- Input power factor improved to 0.99, thus reducing kVA source requirements
- Input Diode rectifiers & magnetics lead to a reliable drive system
- More robust and trouble free than Harmonic Trap filters
- Specified for use on high "Z" Aux-Gen unit
- Lower \$ than Active PWM Rectifier approach

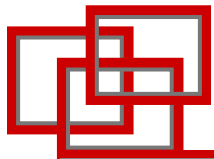

18-Pulse Front-End


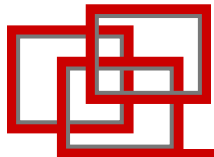
- 18 pulse
 - Diode bridge converter
 - Common DC bus drive
 - Auto-transformer






Active Front-End



- Typical I(THD) of 3 to 5%

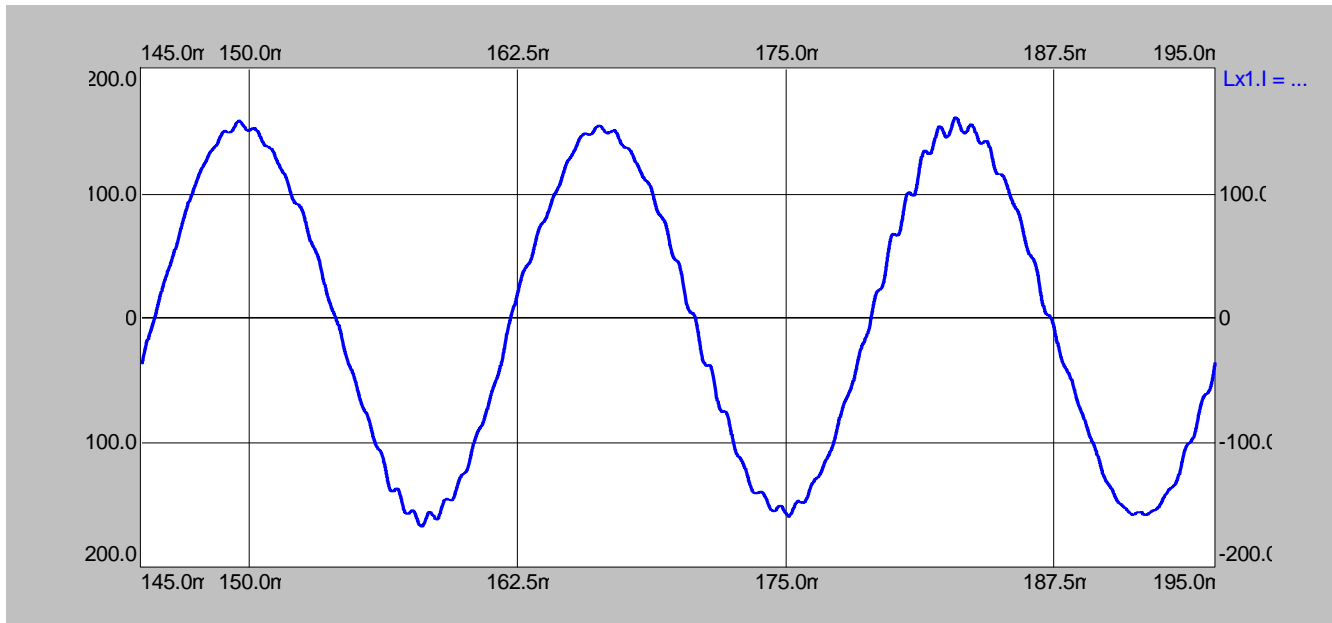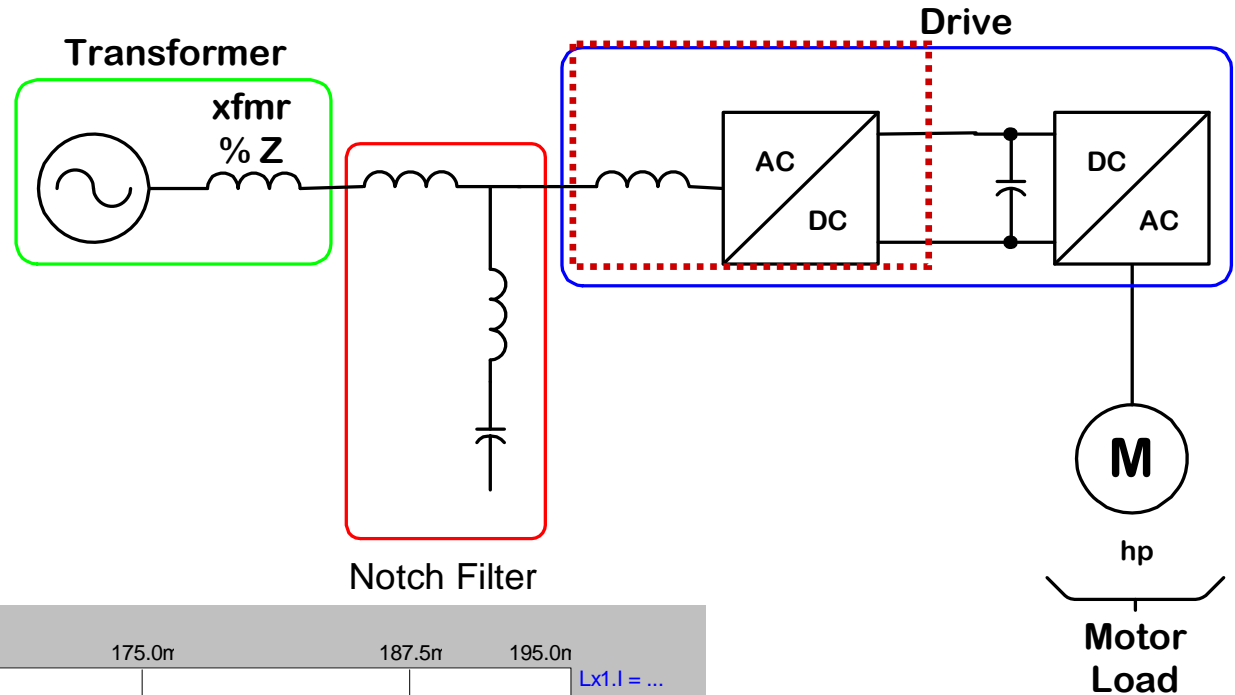


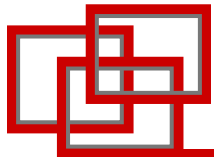


Active Front-End

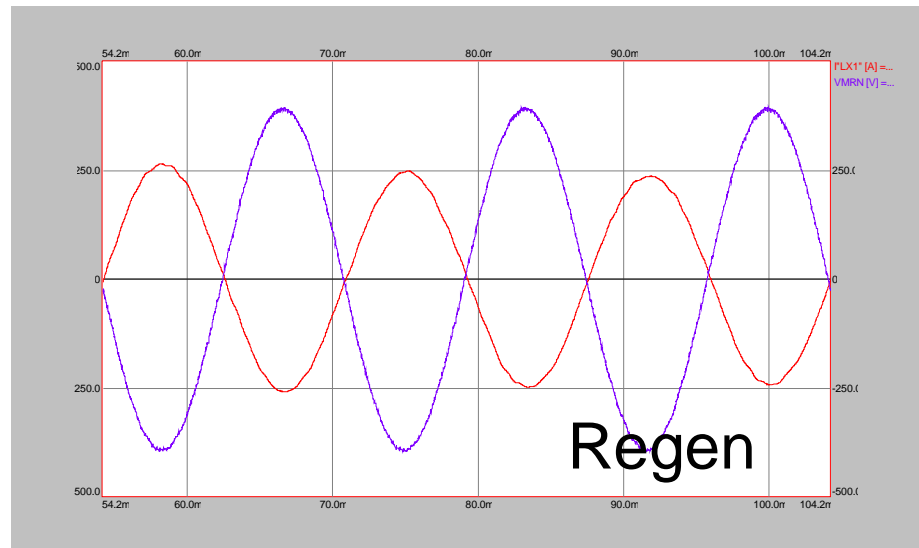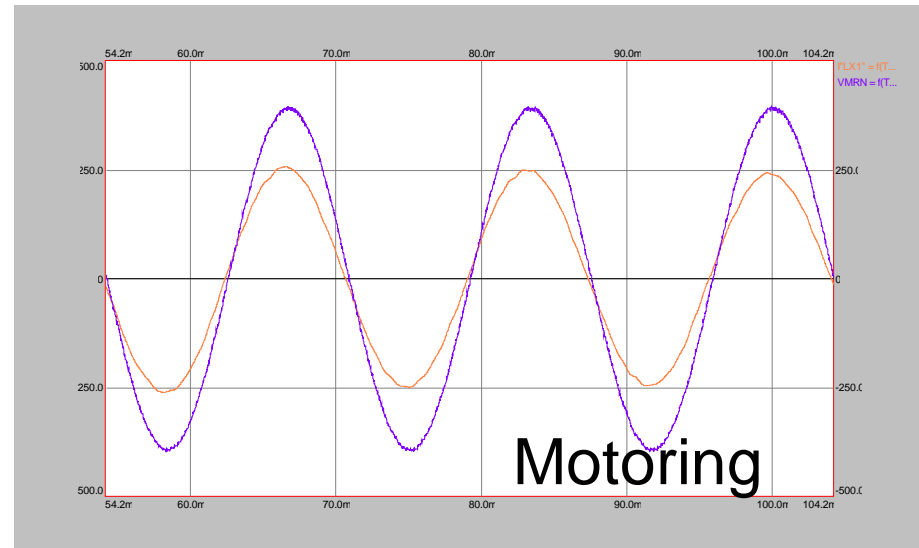
- Serves as Input to Drive(s)
 - Multiple drives on one DC bus
- Regulated DC Bus
 - Ride Through Capability
 - No loss of motor voltage
- Unity Displacement Power Factor
- Low Harmonics
 - IEEE-519
- Regenerative
 - Energy Saving
 - 100% Regenerative Capacity



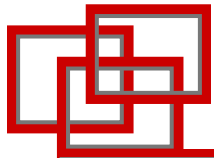

Regenerative AC Drive

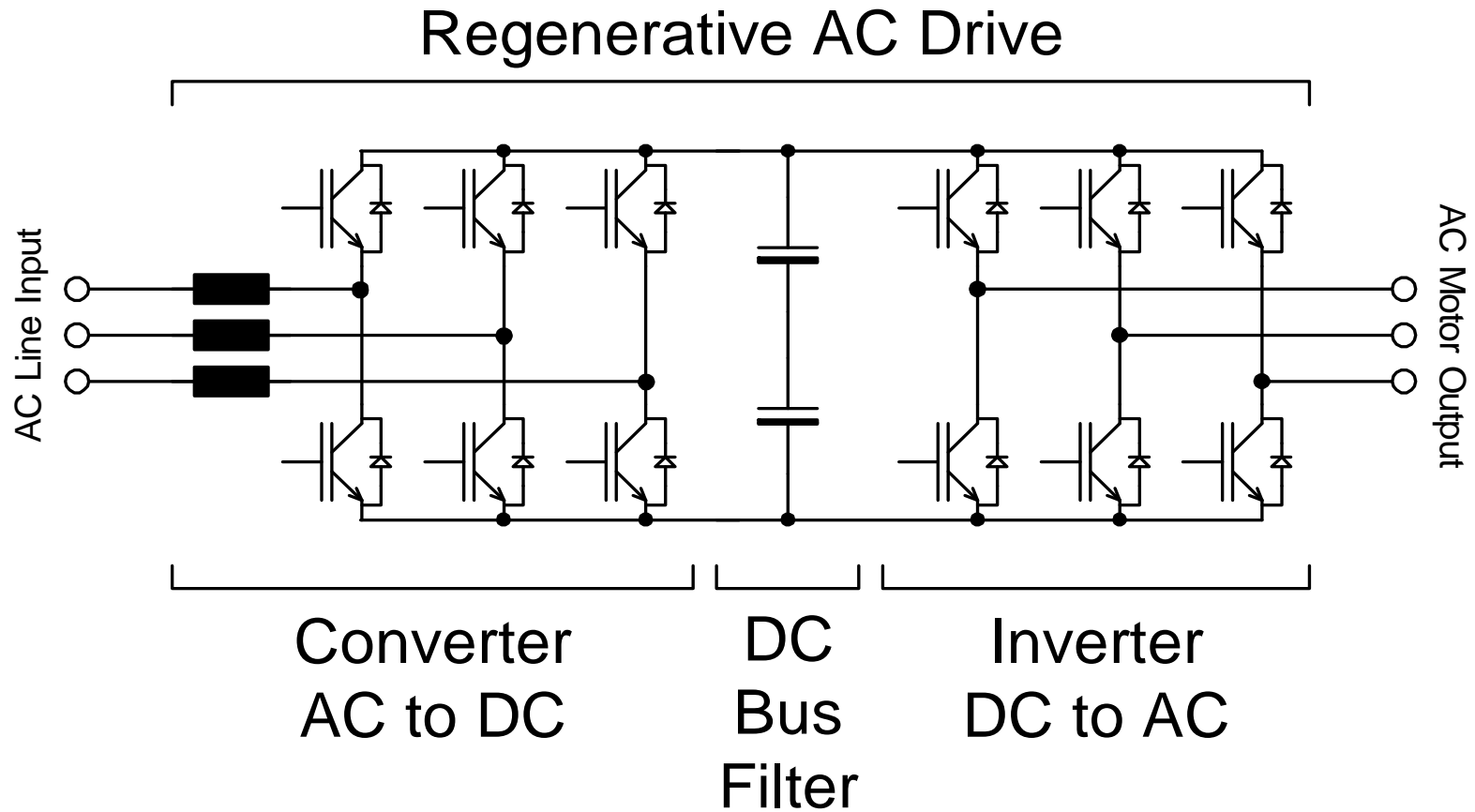

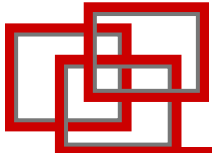


Harmonic Mitigation Technique Active Front End Rectifier


A dual-direction converter that ...


- Supplies forward power to a common DC bus drive system with Sinusoidal input currents
- Regenerates excess power back to the 3-phase AC line with Sinusoidal input currents

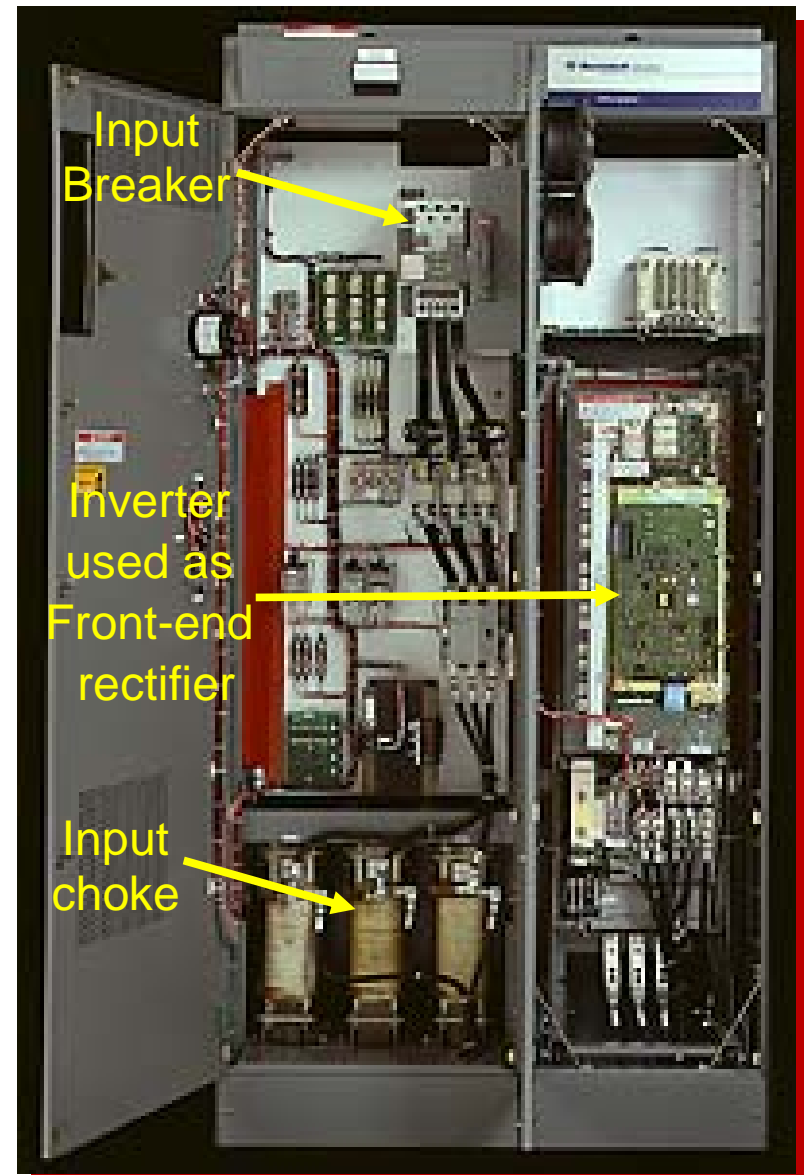Output: 200A DC
Input: 460V AC, 145 kVA
(K-Code)





Liquid Cooled Drive

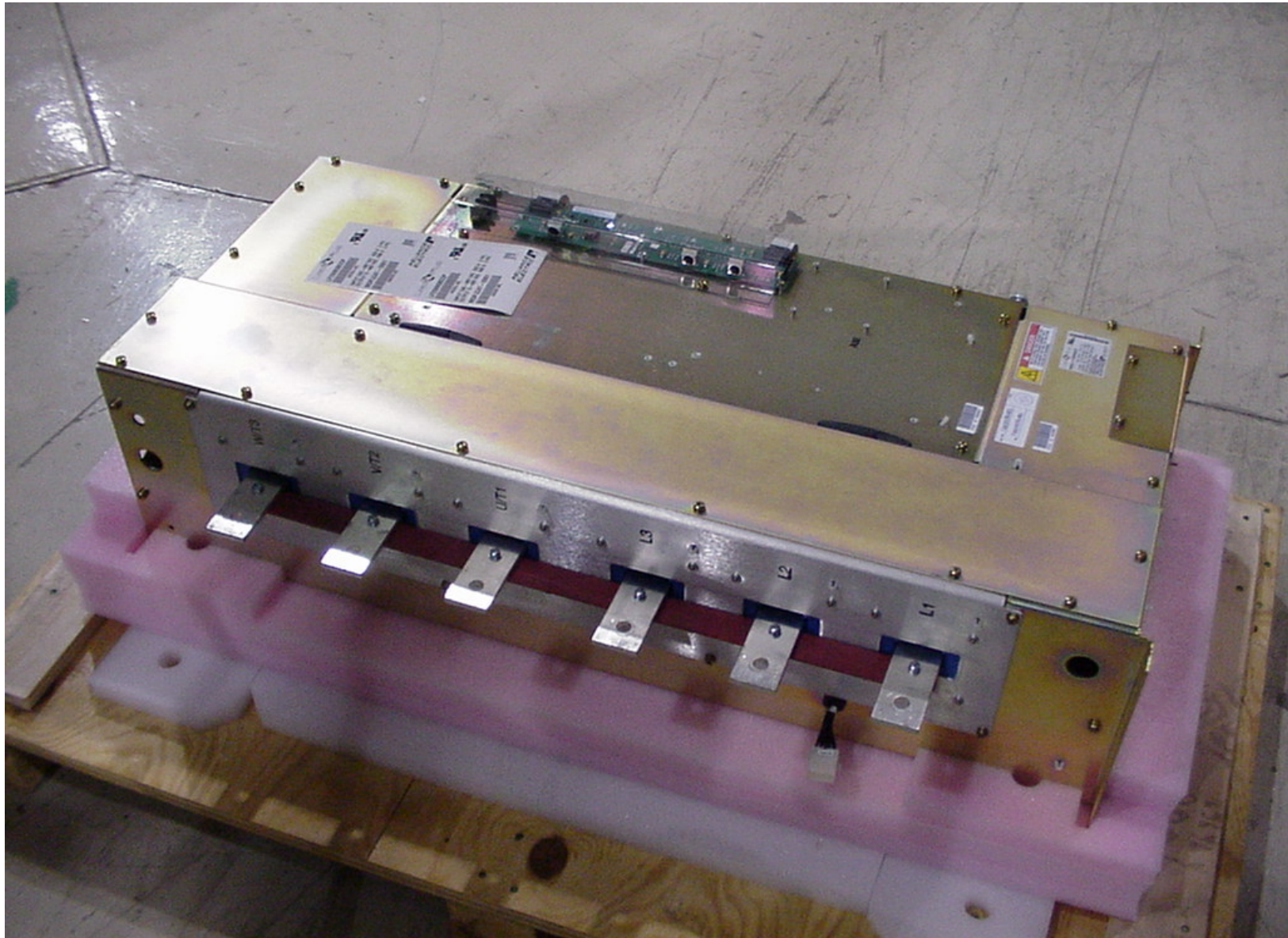

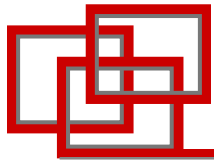



Inverter IGBTs

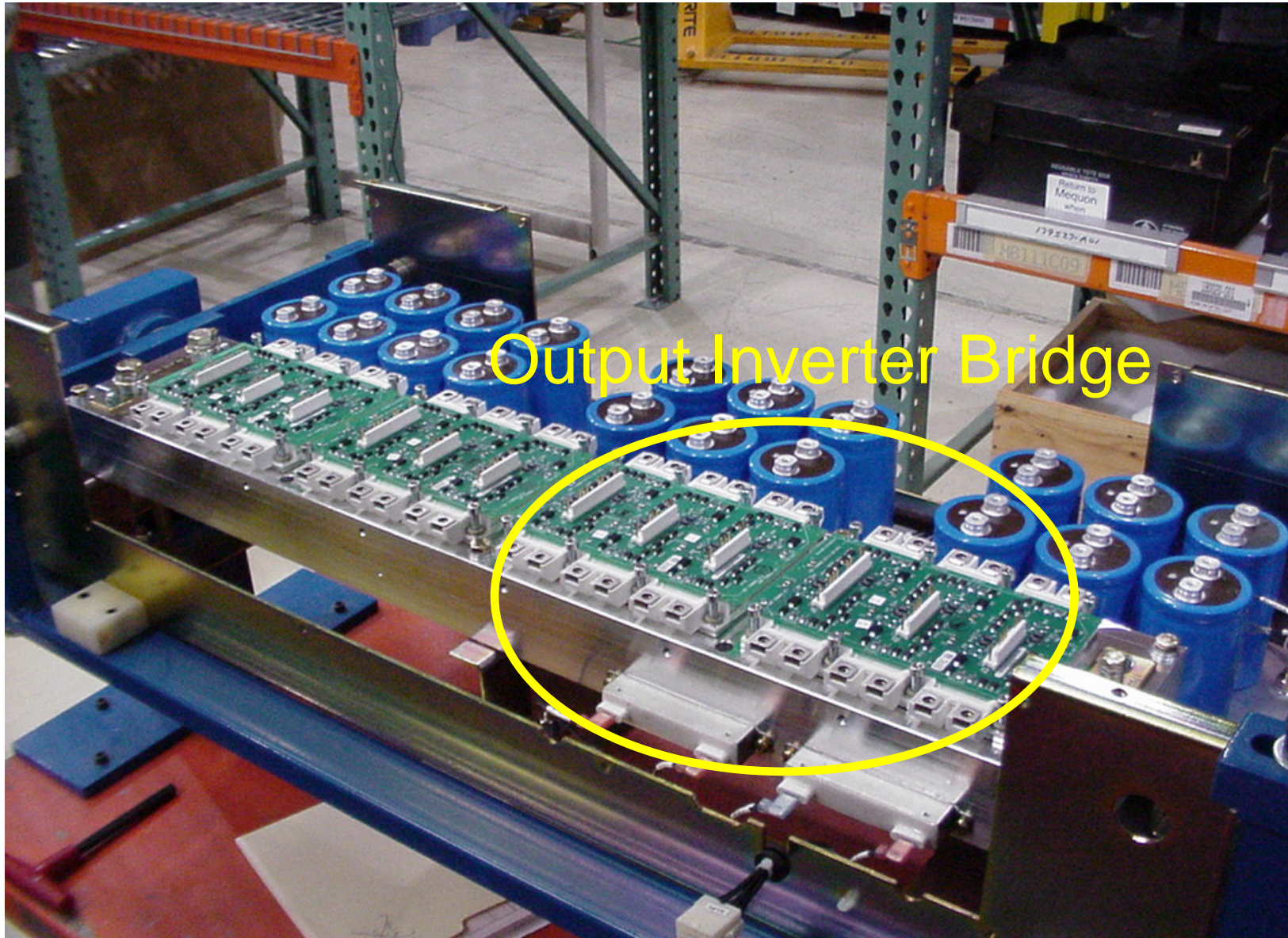

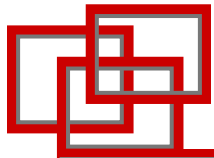


AFE Converter IGBTs

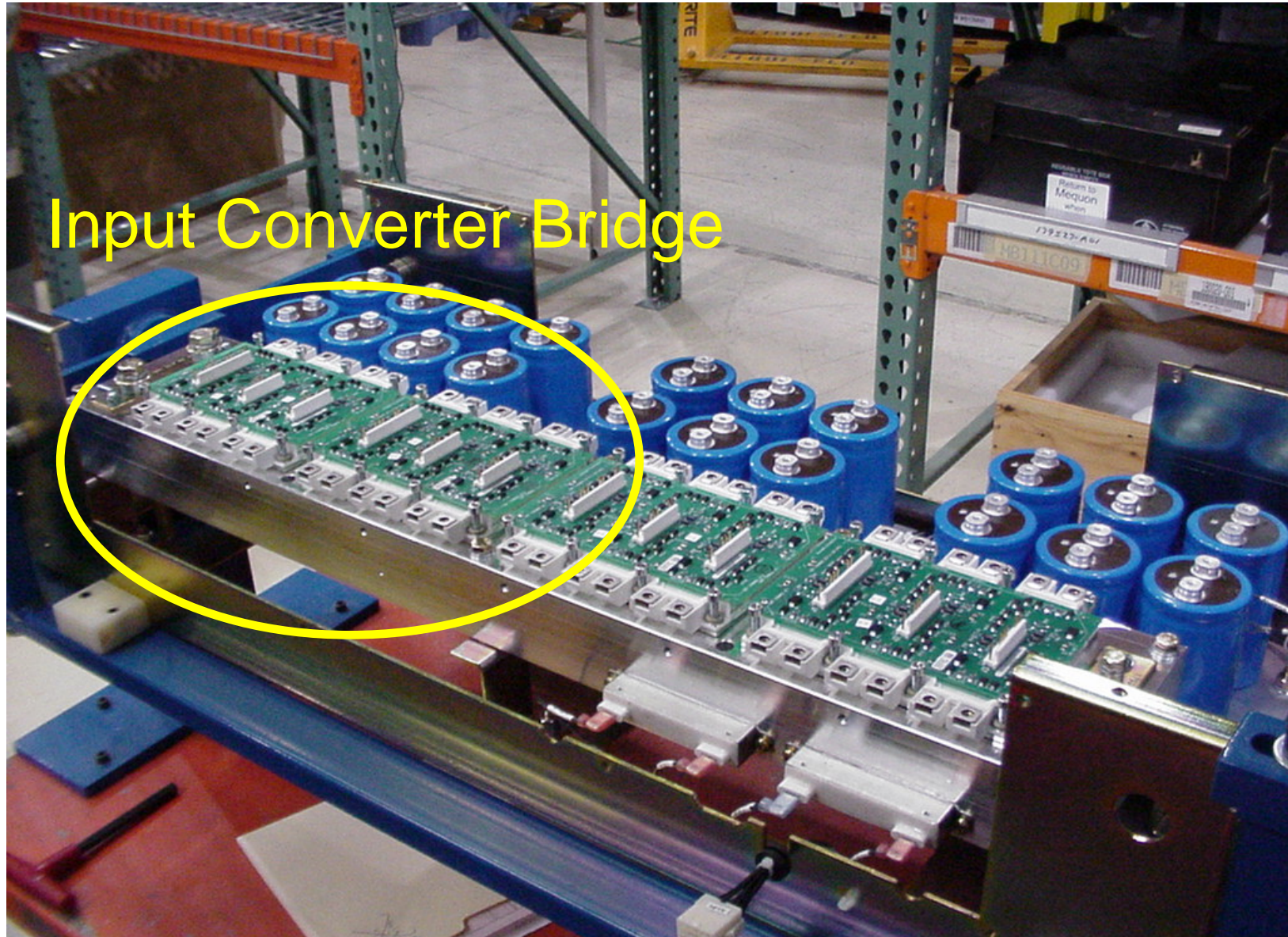

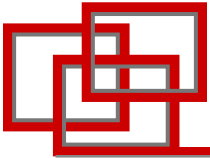

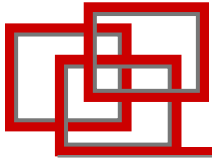**Can we estimate what the
harmonics will be?**



Rockwell Automation Can Help Choose the Right Solution

"I don't know where to start!"

- What is needed?
 - Power distribution drawing showing utility and feed transformer specifications
 - Maximum Short Circuit Current (this figure comes from the utility)
 - Linear and non-linear loads



The screenshot displays the Advanced Harmonic Estimator software interface. It features a central power system diagram with three Power Conditioning Centers (PCC1, PCC2, PCC3) and a Distribution Panel. PCC1 is at the utility xfmr, PCC2 is at the user xfmr, and PCC3 is at the distribution panel. The diagram shows the flow of power from the utility through the transformers to the distribution panel, which then feeds various loads.

Utility Transformer or Generator at PCC1:

50000	kVA 1
8.00	%Z 1
13800	Vsec 1
0	Isc 1

User Transformer at PCC2:

1500	kVA 2
5.75	%Z 2
480	Vsec 2
0	Isc 2

at PCC1 (Intermediate Calculations):

50000	kVA 1
2092	Irated 1
26149	Isc 1
808.3	L, uH1
1.0	K-factor
0.0	% I _{rms} total to I _{rated}
0.0	% thermal rating
0.0	I _{rms} harmonics
0.0	I _{rms} fundamental
0.0	I _{rms} total

at PCC2 (Intermediate Calculations):

1500	kVA 2
1804	Irated 2
31379	Isc 2
23.4	L, uH2
1.0	K-factor
0.0	% I _{rms} total to I _{rated}
0.0	% thermal rating
0.0	I _{rms} harmonics
0.0	I _{rms} fundamental
0.0	I _{rms} total

at PCC3 (Intermediate Calculations):

480	Vsec 3
31379	Isc 3
0.0	L, uH3
0.0	I _{rms} harmonics
0.0	I _{rms} fundamental
0.0	I _{rms} total

Non-Linear Drive Load (Vertical Column):


0	feet to panel	6 pulse unbuffered drive without line reactor	0	total hp
0	feet to panel	6 pulse buffered drive without line reactor	0	total hp
0	feet to panel	6 pulse buffered drive with 3% line reactor	0	total hp
0	feet to panel	6 pulse buffered drive with 5% line reactor	0	total hp
0	feet to panel	6 pulse buffered drive with basic harmonic filter	0	total hp
0	feet to panel	12 pulse buffered drive with auto xfmr	0	total hp
0	feet to panel	12 pulse buffered drive with iso xfmr	0	total hp
0	feet to panel	18 pulse buffered drive with auto xfmr	0	total hp
0	feet to panel	18 pulse buffered drive with iso xfmr	0	total hp
0	feet to panel	Custom	0	I _{fund} at FL

Design Checks: (blank if no issues)


26148.9	Isc/Load	Limit
0.0	% V(THD)	20.0
0.0	% I(TDD)	20.0
YES	IEEE special (3% V _{thd})	
YES	IEEE general (5% V _{thd})	
YES	IEEE dedicated (10% V _{thd})	

Cell Key:


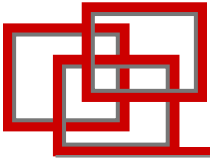
- Green box: data entry
- Light blue box: intermediate calc
- Yellow box: harmonic results



Harmonic Mitigation: Comparisons

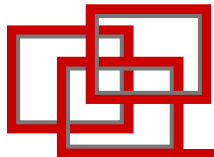


Performance Charts

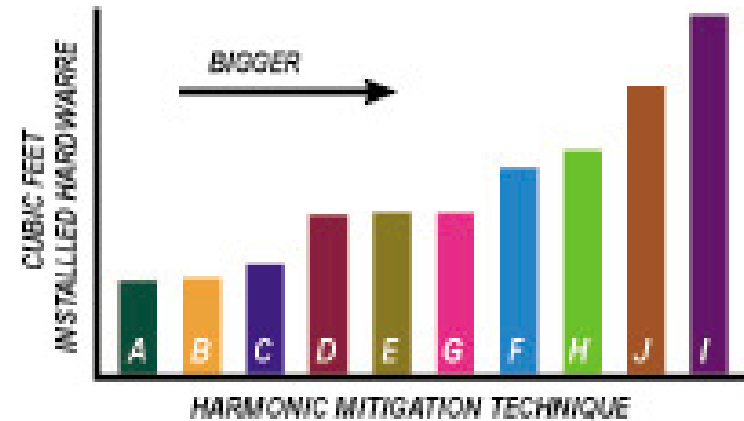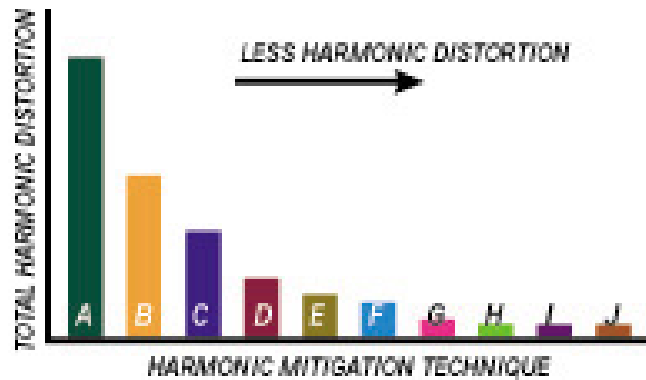


Legend

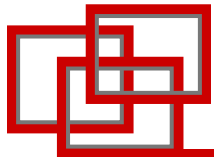
- A. 6-pulse, no link choke
- B. 6-pulse, with link choke
- C. Input line reactor
- D. Tuned and non-tuned filters
- E. 12-pulse with auto transformer
- F. 12-pulse with isolation transformer
- G. 18-pulse with auto transformer
- H. 18-pulse with isolation transformer
- I. Regenerative active front end
- J. Active power filter





Harmonic Mitigation Comparisons - Costs

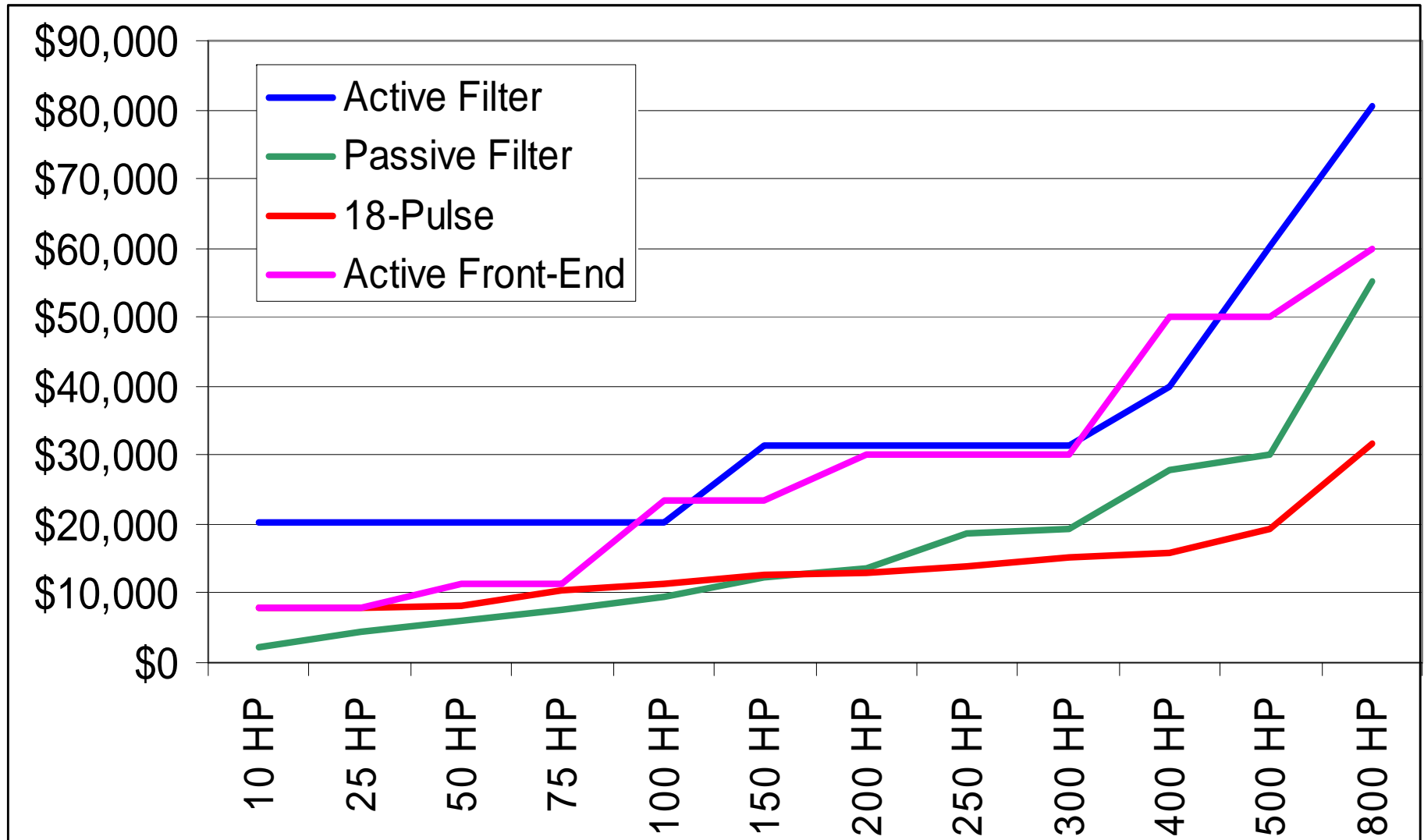

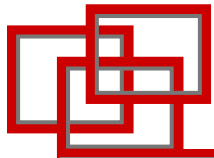

Solutions Check-List

Harmonic Mitigation Solutions Check-List	6-Pulse Drive		18-Pulse Drive		Passive Filter		Active Filter		Active Front-End	
	Typical Ithd									
Typical Ithd	20 - 45%		4.5 - 6%		5 - 8%		3 - 5%		3 - 5%	
Meet IEEE Special Applications	No	✗	Yes	✓	Marginal		Yes	✓	Yes	✓
Meet IEEE General Applications	No	✗	Yes	✓	Yes	✓	Yes	✓	Yes	✓
Meet IEEE Dedicated Applications	Yes	✓	Yes	✓	Yes	✓	Yes	✓	Yes	✓
Effect of 1% Voltage Unbalance	Large	✗	Moderate		Minimal	✓	Minimal	✓	Minimal	✓
Potential Low DC Bus	No		No		Yes	?	No		No	
Potential System Resonance	No		No		Yes	?	No		No	
Typical Total Power Factor, no / full load	0.75 - 0.95		0.90 - 0.99	✓	0.3 - 1 lead	?	0.90 - 0.99	✓	0.8 - 1 lead	
Efficiency	97%	✓	96.5%	✓	96.5%	✓	96%		96 - 97.5%	
Cost Effective	Good	✓	>150hp	✓	<150hp	✓	Large Sys		Regen, MV	
Overall Size (relative to 6-P Drive)	1.0		3.3		2 - 6		3.5 - 5		1.5 - 2.5	✓
Reliability	High	✓	High	✓	Medium		Medium		Medium	



Good



Need to confirm application




May not meet IEEE 519

LISTEN.
THINK.
SOLVE.SM


Questions?

ALLEN-BRADLEY • ROCKWELL SOFTWARE • DODGE • RELIANCE ELECTRIC

**Rockwell
Automation**

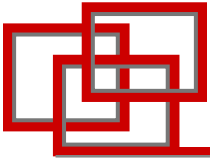


Wrap-Up

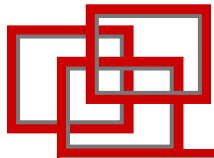


Practical Aids for Harmonic Compliance

- Take time to understand the benefits and drawbacks of each type of mitigation solution to assure you meet the requirements of the application and that you can live with any negative effects created by the chosen harmonic solution.
- Identify the required PCC and apply techniques most cost effective for that location.
- Perform a preliminary harmonic analysis and explore the effects of using various harmonic mitigation methods.
- Add a line reactor (or DC link choke if possible) to any unbuffered 6-pulse drive or group of drives.

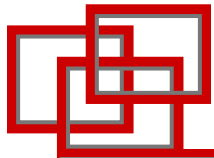


Practical Aids for Harmonic Compliance

- Design the system to isolate linear and non-linear loads and create two systems with 5% and 10% voltage limits.
- For passive filters on generator power, select a filter with a dropout contactor terminal block for the filter capacitors. This will limit the leading power factor under no-load operation and stand-by operation.
- Never use power factor correction capacitors at the input (or output) of a drive.

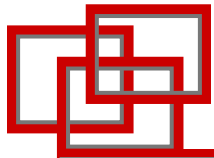

Practical Aids for Harmonic Compliance

- Consider use of an active filter on a multiple drive system or MCC lineup to correct for harmonic distortion.
- Consider an active front end if the application requires regenerative operation and harmonic compliance.
- When conducting a drives-based harmonic analysis, establishing the PCC at any point other than where the sharing of utility power occurs is not consistent with the intent of IEEE519-1992 and may lead to the purchase of unnecessary equipment.

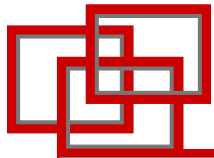

Market Trends

- The 18 Pulse market is firmly established.
- Passive filter are evolving. Recent new designs have surfaced with very good performance. System resonance with multiple filters needs investigation. Suitable for smaller horsepower <100
- Active Filters are technically viable but *right now* are a more costly solution for most projects.
- Active Filters fare better on large projects with the PCC specified at transformer secondary.
- The price of copper and iron is going up while the price of power electronics is coming down.

LISTEN.
THINK.
SOLVE.SM

Questions?

ALLEN-BRADLEY • ROCKWELL SOFTWARE • DODGE • RELIANCE ELECTRIC

Rockwell
Automation